

EN 206: Power Electronics and Machines

dc-dc Converters

Suryanarayana Doolla


Department of Energy Science and Engineering
Indian Institute of Technology Bombay
email: suryad@iitb.ac.in

March 12, 2014

Lecture Organization - Modules


- Introduction and Power Semiconductor Switches
- Module 1: Transformers
- Module 2: AC/DC converter / Rectifier
- Module 3: DC machines and Drives
- Module 4: DC/DC converter
- Module 5: Induction Machine
- Module 6: DC/AC converter / Inverter
- Module 7: AC/AC converter / Cyclo converter
- Module 8: Synchronous Machine
- Module 9: Special Topics: Machines, HVDC, APF

Linear Power Supply

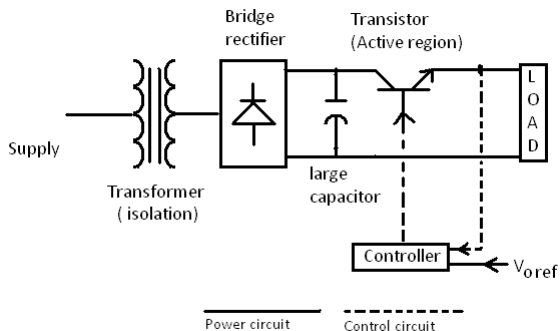


- Require bulky transformer

Linear Power Supply

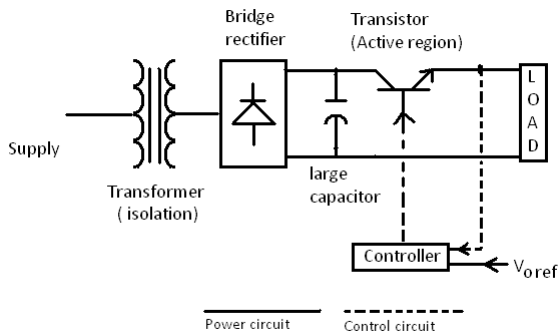


- Require bulky transformer
- Efficiency is very low (30-60%), and preferred for power supply rating $< 25W$

Switched Mode Power Supply (SMPS)

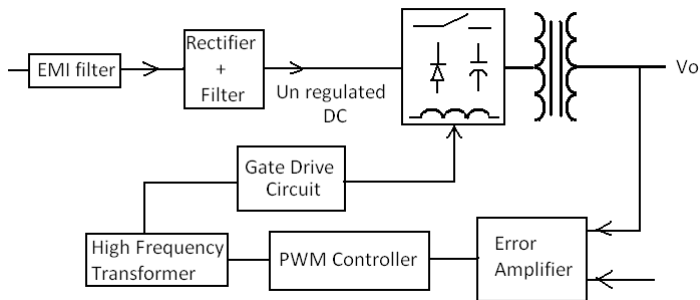


- Reduced size of transformer

Switched Mode Power Supply (SMPS)

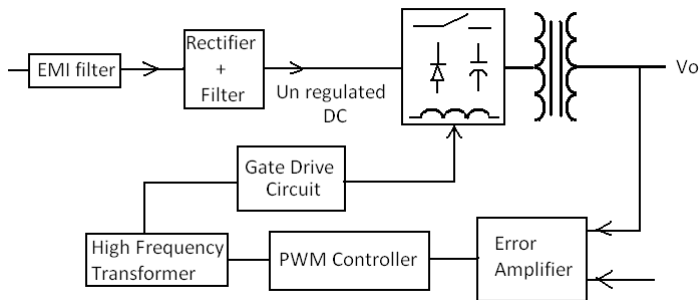

- Reduced size of transformer
- High efficiency (70-90%)

Switched Mode Power Supply (SMPS)

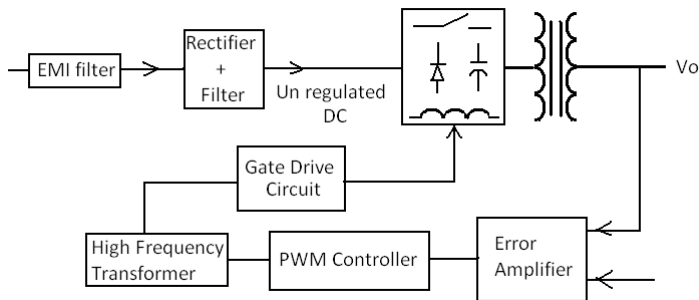

- Reduced size of transformer
- High efficiency (70-90%)
- Transistor operated in on/off mode has large power handling capability compared to one in linear mode

dc-dc Converter - Classification

- Direct Converters (Non-Isolated)

dc-dc Converter - Classification

- Direct Converters (Non-Isolated)
 - Buck, Boost

dc-dc Converter - Classification

- Direct Converters (Non-Isolated)
 - Buck, Boost
- Derived Converters (Non-Isolated)

dc-dc Converter - Classification

- Direct Converters (Non-Isolated)
 - Buck, Boost
- Derived Converters (Non-Isolated)
 - Buck-Boost, Cuk

dc-dc Converter - Classification

- Direct Converters (Non-Isolated)
 - Buck, Boost
- Derived Converters (Non-Isolated)
 - Buck-Boost, Cuk
- Full Bridge dc-dc Converters (Non-Isolated)

dc-dc Converter - Classification

- Direct Converters (Non-Isolated)
 - Buck, Boost
- Derived Converters (Non-Isolated)
 - Buck-Boost, Cuk
- Full Bridge dc-dc Converters (Non-Isolated)
 - Bi Polar voltage switching, Uni Polar voltage switching

dc-dc Converter - Classification

- Direct Converters (Non-Isolated)
 - Buck, Boost
- Derived Converters (Non-Isolated)
 - Buck-Boost, Cuk
- Full Bridge dc-dc Converters (Non-Isolated)
 - Bi Polar voltage switching, Uni Polar voltage switching
- Isolated



dc-dc Converter - Classification

- Direct Converters (Non-Isolated)
 - Buck, Boost
- Derived Converters (Non-Isolated)
 - Buck-Boost, Cuk
- Full Bridge dc-dc Converters (Non-Isolated)
 - Bi Polar voltage switching, Uni Polar voltage switching
- Isolated
 - Unidirectional core excitation (Flyback, Forward)

dc-dc Converter - Classification

- Direct Converters (Non-Isolated)
 - Buck, Boost
- Derived Converters (Non-Isolated)
 - Buck-Boost, Cuk
- Full Bridge dc-dc Converters (Non-Isolated)
 - Bi Polar voltage switching, Uni Polar voltage switching
- Isolated
 - Unidirectional core excitation (Flyback, Forward)
 - Bidirectional core excitation (Push-Pull, Half Bridge, Full bridge)

Pulse Width Modulation (PWM)

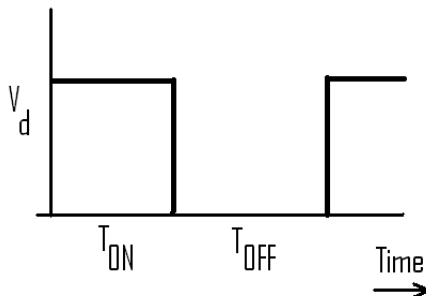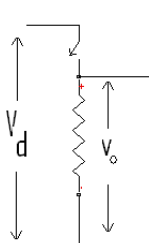

$$V_0 = \frac{1}{T_s} \int_0^{t_{ON}} V_d dt + \frac{1}{T_s} \int_0^{t_{ON}} 0 dt$$

$$V_0 = DV_s$$

D is defined as the ratio of on time to total time and is given by $D = \frac{T_{on}}{T_s}$

Pulse Width Modulation

- Constant Frequency

Pulse Width Modulation

- Constant Frequency
 - Commonly employed

Pulse Width Modulation

- Constant Frequency
 - Commonly employed
- Variable Frequency

Pulse Width Modulation

- Constant Frequency
 - Commonly employed
- Variable Frequency
 - Difficulty in filtering out harmonics of output waveform

Pulse Width Modulation

- Constant Frequency
 - Commonly employed
- Variable Frequency
 - Difficulty in filtering out harmonics of output waveform
 - Generally employed using thyristors

Pulse Width Modulation

- Constant Frequency
 - Commonly employed
- Variable Frequency
 - Difficulty in filtering out harmonics of output waveform
 - Generally employed using thyristors
- Two Modes of operation



Pulse Width Modulation

- Constant Frequency
 - Commonly employed
- Variable Frequency
 - Difficulty in filtering out harmonics of output waveform
 - Generally employed using thyristors
- Two Modes of operation
 - Continuous current mode

Pulse Width Modulation

- Constant Frequency
 - Commonly employed
- Variable Frequency
 - Difficulty in filtering out harmonics of output waveform
 - Generally employed using thyristors
- Two Modes of operation
 - Continuous current mode
 - Dis-Continuous current mode

Pulse Generation

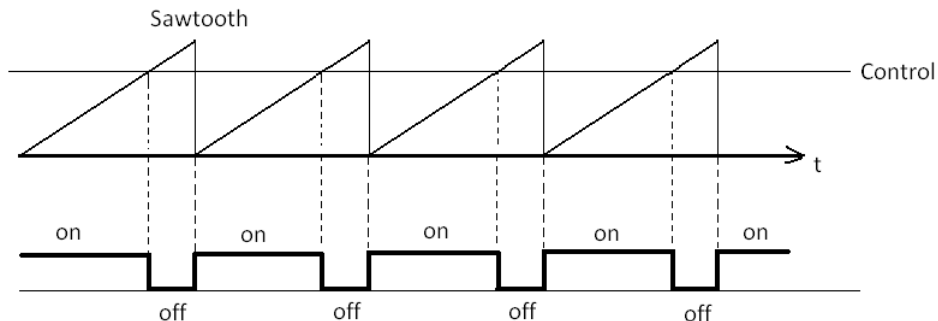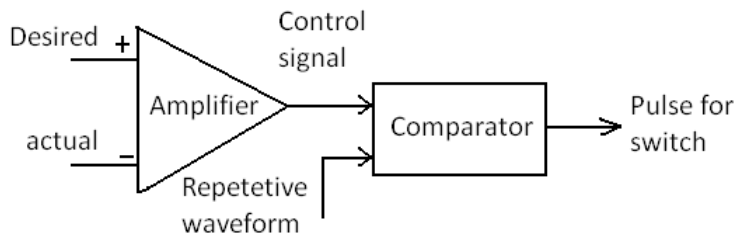

dc-dc Converter - Steady state analysis

- The converters are analyzed in steady state.

dc-dc Converter - Steady state analysis

- The converters are analyzed in steady state.
- Switches are considered as ideal, the losses in inductive and capacitive elements are neglected.

dc-dc Converter - Steady state analysis

- The converters are analyzed in steady state.
- Switches are considered as ideal, the losses in inductive and capacitive elements are neglected.
- The dc input voltage to the converters is assumed to have zero/low impedance.


dc-dc Converter - Steady state analysis

- The converters are analyzed in steady state.
- Switches are considered as ideal, the losses in inductive and capacitive elements are neglected.
- The dc input voltage to the converters is assumed to have zero/low impedance.
- Switched mode converters utilize one or more switches to convert input voltage from one state to other at the output

dc-dc Converter - Steady state analysis

- The converters are analyzed in steady state.
- Switches are considered as ideal, the losses in inductive and capacitive elements are neglected.
- The dc input voltage to the converters is assumed to have zero/low impedance.
- Switched mode converters utilize one or more switches to convert input voltage from one state to other at the output
- The frequency of repetitive waveform is kept constant and amplitude of control signal is varied.


Buck converter

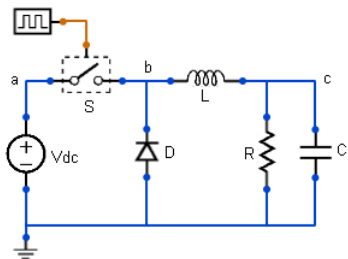

V_s = Supply Voltage,
 V_0 = Output Voltage,
 V_L = Inductor Voltage = $V_s - V_0$

- The average output voltage is less than the input voltage V_d


Buck converter

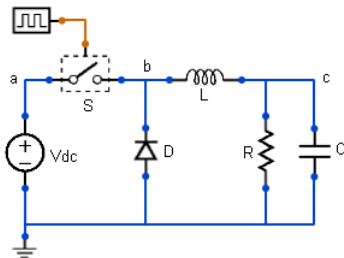

V_s = Supply Voltage,
 V_0 = Output Voltage,
 V_L = Inductor Voltage = $V_s - V_0$

- The average output voltage is less than the input voltage V_d
- The average output voltage varies linearly with control voltage

Buck converter

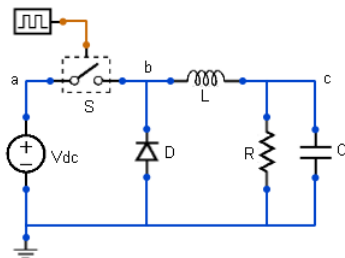


V_s = Supply Voltage,
 V_0 = Output Voltage,
 V_L = Inductor Voltage = $V_s - V_0$

- The average output voltage is less than the input voltage V_d
- The average output voltage varies linearly with control voltage
- The filter capacitor is assumed to be high so that the output voltage is more or less constant

Buck converter-CC Mode

Inductor Voltage and Current

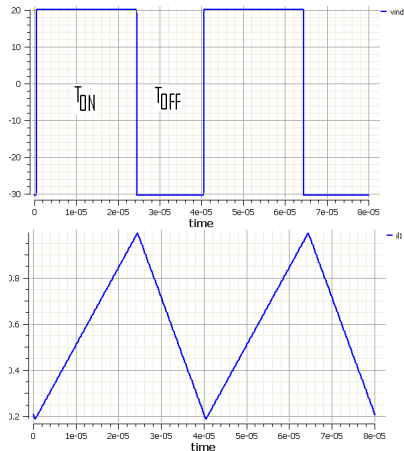


Analysis

When the switch is ON, Inductor current is rising

Buck converter-CC Mode

Inductor Voltage and Current

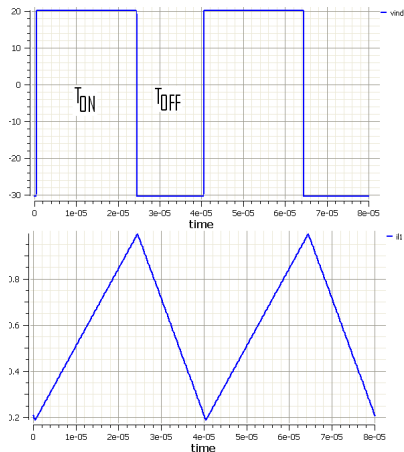



Analysis

When the switch is ON, Inductor current is rising

When the switch is OFF, Inductor current is falling

Buck converter-CC Mode

Inductor Voltage and Current

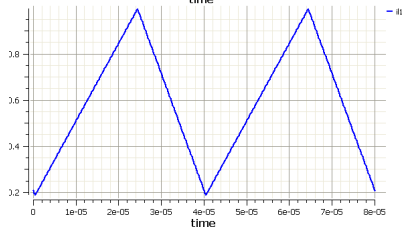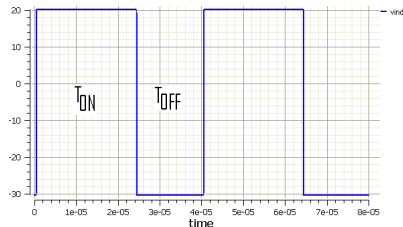

Analysis

When the switch is ON, Inductor current is rising

When the switch is OFF, Inductor current is falling

$$V_L = \frac{1}{T_s} \int_0^{T_{on}} (V_d - V_0).dt$$

$$+ \frac{1}{T_s} \int_{T_{on}}^{T_s} -(V_0).dt$$

Buck converter-CC Mode

$$V_L = \frac{1}{T_s} \int_0^{T_{on}} (V_d - V_0).dt + \frac{1}{T_s} \int_{T_{on}}^{T_s} -(V_0).dt$$

$$V_L = \frac{T_{on}}{T_s} (V_d - V_0) - \frac{V_0}{T_s} (T_s - T_{on})$$

Buck converter-CC Mode

$$V_L = \frac{1}{T_s} \int_0^{T_{on}} (V_d - V_0).dt + \frac{1}{T_s} \int_{T_{on}}^{T_s} -(V_0).dt$$

$$V_L = \frac{T_{on}}{T_s} (V_d - V_0) - \frac{V_0}{T_s} (T_s - T_{on})$$

The average voltage across inductor in a cycle is zero.

$$V_0 = \frac{T_{on}}{T_s} V_d$$

Buck converter-CC Mode

$$V_L = \frac{1}{T_s} \int_0^{T_{on}} (V_d - V_0).dt + \frac{1}{T_s} \int_{T_{on}}^{T_s} -(V_0).dt$$

$$V_L = \frac{T_{on}}{T_s} (V_d - V_0) - \frac{V_0}{T_s} (T_s - T_{on})$$

The average voltage across inductor in a cycle is zero.

$$V_0 = \frac{T_{on}}{T_s} V_d$$

$$V_0 = DV_d$$

Buck converter-CC Mode

$$V_L = \frac{1}{T_s} \int_0^{T_{on}} (V_d - V_0).dt + \frac{1}{T_s} \int_{T_{on}}^{T_s} -(V_0).dt$$

$$V_L = \frac{T_{on}}{T_s} (V_d - V_0) - \frac{V_0}{T_s} (T_s - T_{on})$$

The average voltage across inductor in a cycle is zero.

$$V_0 = \frac{T_{on}}{T_s} V_d$$


$$V_0 = DV_d$$

Assuming a lossless circuit,

$$\frac{I_d}{I_0} = \frac{V_0}{V_d} = D$$

Boundary Condition -CCM and DCM

Inductor Current and Voltage

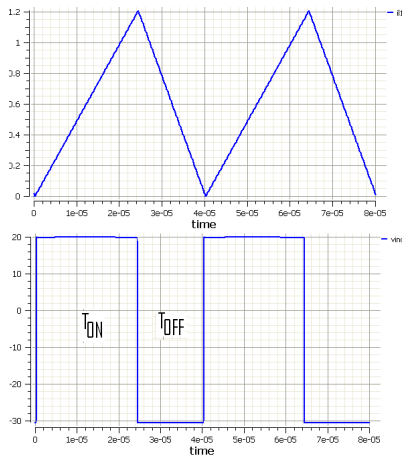

Analysis

$$I_{LB} = \frac{1}{2} I_{L,peak}$$

$$\Rightarrow I_{LB} = \frac{1}{2} \frac{V_d - V_0}{L} T_{on}$$

$$\Rightarrow I_{LB} = \frac{DT_s}{2L} (V_d - V_0)$$


also,

$$V_0 = DV_d$$

$$\Rightarrow I_{LB} = \frac{V_d T_s}{2L} [D(1 - D)]$$

Boundary Condition

Inductor Current with duty cycle

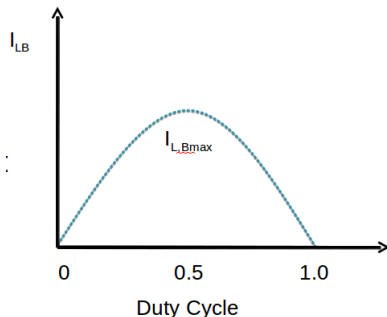


Analysis

The inductor current is minimum at $D=0$ and $D=1$, and is maximum at $D=0.5$, also

$$I_{L,Bmax} = \frac{V_d T_s}{8L}$$

Boundary Condition

Inductor Current with duty cycle

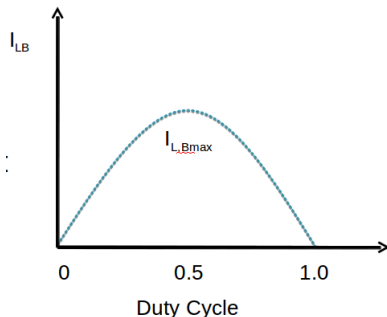

Analysis

The inductor current is minimum at $D=0$ and $D=1$, and is maximum at $D=0.5$, also

$$I_{L,Bmax} = \frac{V_d T_s}{8L}$$

If we consider that the average current through the capacitor is zero then $I_{OB} = I_{LB}$

If the current is less than I_{OB} or I_{LB} , it is said to be discontinuous in nature i.e., i_L become discontinuous.

Buck Converter - DCM

- Either input voltage or output voltage is constant

Buck Converter - DCM

- Either input voltage or output voltage is constant
- DCM with constant input voltage (V_d)

Buck Converter - DCM

- Either input voltage or output voltage is constant
- DCM with constant input voltage (V_d)

- Boundary Condition:

$$I_{LB} = \frac{V_d T_s}{2L} [D(1 - D)], I_{L,Bmax} = \frac{V_d T_s}{8L}, I_{L,B} = 4I_{LBmax} D(1 - D)$$

Buck Converter - DCM

- Either input voltage or output voltage is constant
- DCM with constant input voltage (V_d)


- Boundary Condition:

$$I_{LB} = \frac{V_d T_s}{2L} [D(1 - D)], I_{L,Bmax} = \frac{V_d T_s}{8L}, I_{L,B} = 4I_{LBmax} D(1 - D)$$

- Assume that initially the converter is operated at edge of CCM and the output load power is decreased, i.e., “R” increases and hence “ i_L ” decreases introducing discontinuity in the current waveform

Buck Converter - DCM

Inductor Current with duty cycle

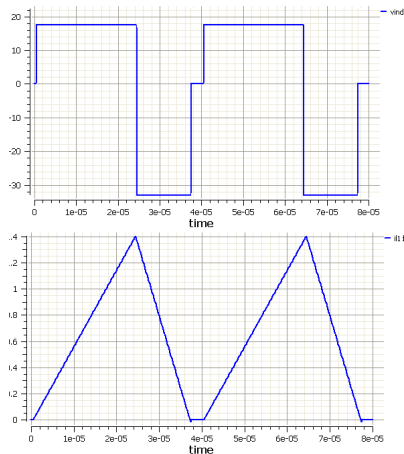

Analysis

Average voltage across inductor in zero.

$$(V_d - V_0)DT_s + (-V_0)\Delta_1 T_s = 0$$

$$\Rightarrow V_d D \cdot T_s = T_s V_0 (D + \Delta_1)$$


$$\Rightarrow V_0 = \frac{D}{D + \Delta_1} V_d$$

The unknown parameter (Δ_1) can be derived in terms of known parameters,

$$V_0 = \frac{D^2}{D^2 + \frac{l_0}{I_{LBmax} \times \frac{1}{4}}} \times V_d$$

$$\Delta_1 = \frac{l_0}{I_{LBmax} \times \frac{1}{4D}}$$

Boundary Condition

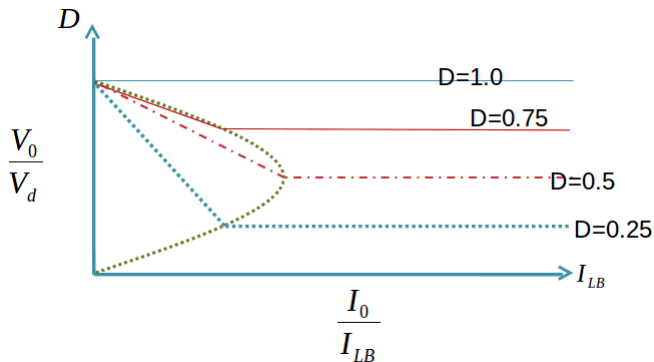

- Boundary between CCM and DCM is given by dotted line.

Output Ripple -CCM

$$\Delta V_0 = \frac{\Delta Q}{C} = \frac{1}{C} \times \frac{1}{2} \times \frac{\Delta I_L}{2} \times \frac{T_s}{2}$$

Also during the turnoff t_{off}

$$\Delta I_L = \frac{V_0}{L}(1-D)T_s; \quad \Delta V_0 = \frac{T_s V_0}{8LC}(1-D)T_s$$

$$\frac{\Delta V_0}{V_0} = \frac{1}{8} T_s^2 \frac{1}{LC}(1-D); \quad \frac{\Delta V_0}{V_0} = \frac{\pi^2}{2}(1-D) \left(\frac{f_c}{f_s} \right)^2$$

Where f_c is the corner frequency given by $f_c = \frac{1}{2\pi\sqrt{LC}}$

Comparison of Converters

Converter	Output Voltage	Boundary Condition
Buck	$V_0 = DV_d$	$I_{LB} = \frac{V_d T_s}{2L} [D(1 - D)]$
Boost	$V_0 = \frac{D}{1-D} V_d$	$I_{OB} = \frac{V_o T_s}{2L} [D(1 - D)^2]$

Summary

- DC/DC Converters
 - Introduction to DC/DC Converters.
 - Linear and Switched Mode Amplifiers.
 - Buck Converter (CCM and DCM, Boundary Condition).

Next Class

- DC/DC Converter - Boost, Buck-Boost Converter

For Further Reading:

- Power Electronics: Converters, Applications, and Design: N. Mohan, T. M. Undeland, W. P. Robbins, John Wiley and Sons.
- Power electronics and motor drives: advances and trends: Bimal K Bose. Pearson Education.