



EN 206 – Power Electronics and Machines


Prof. Suryanarayana Doolla

DC-DC Converters

- ❖ Isolated Converters
 - ✓ Flyback Converter
 - ✓ Forward Converter
- ❖ Bi Polar Voltage Switching
- ❖ Uni Polar Voltage Switching

POWER SUPPLY


- Linear Power supply

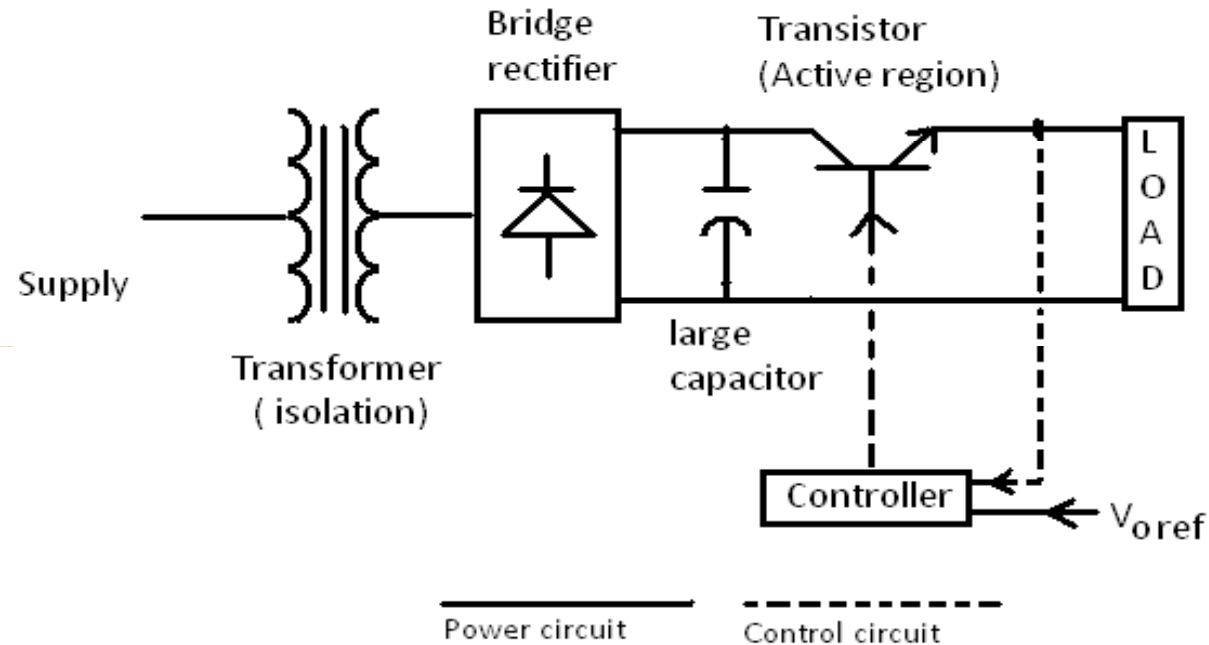

- Require bulky transformer
- Efficiency is very low (30-60%), and preferred for power supply rating $< 25W$

POWER SUPPLY

- Switched Mode Power Supply

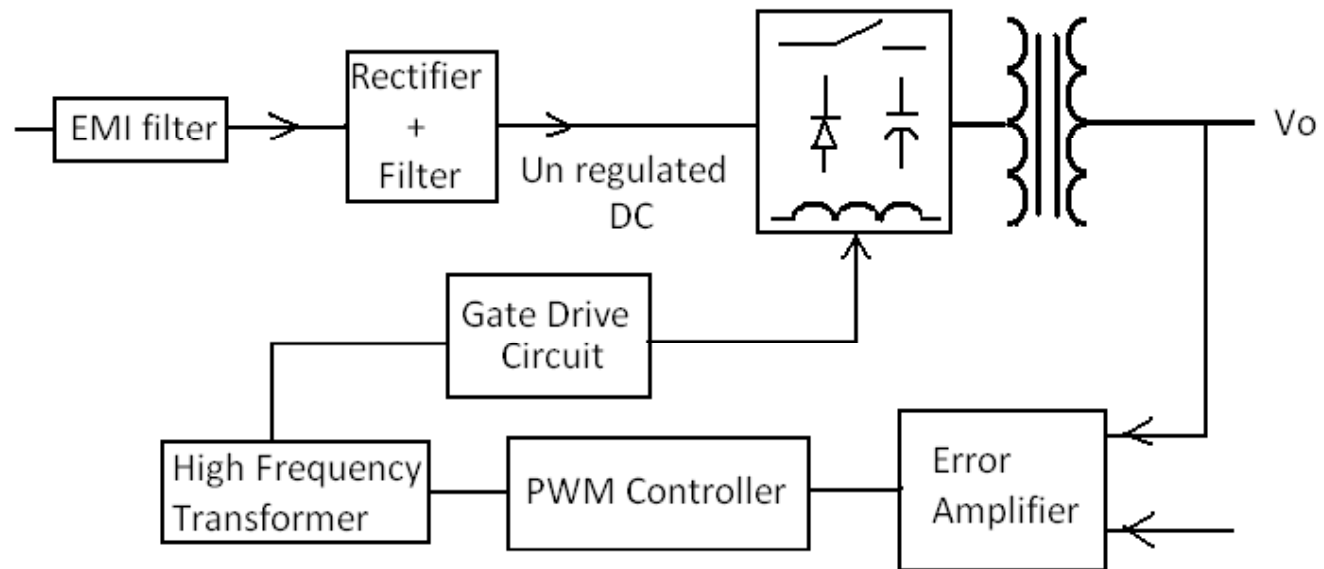

- Reduced size of transformer
- High efficiency (70-90%)
- Transistor operated in on/off mode has large power handling capability compared to one in linear mode




dc-dc Converters

- Direct Converters (Non-Isolated)
 - Buck
 - Boost
- Derived Converters (Non-Isolated)
 - Buck-Boost
 - Cuk
- Full Bridge dc-dc Converters (Non-Isolated)
 - Bi Polar voltage switching
 - Uni Polar voltage switching
- Isolated
 - Unidirectional core excitation
 - Flyback
 - Forward
 - Bidirectional core excitation
 - Push-Pull
 - Half Bridge
 - Full bridge

DC-DC Converter with Isolation

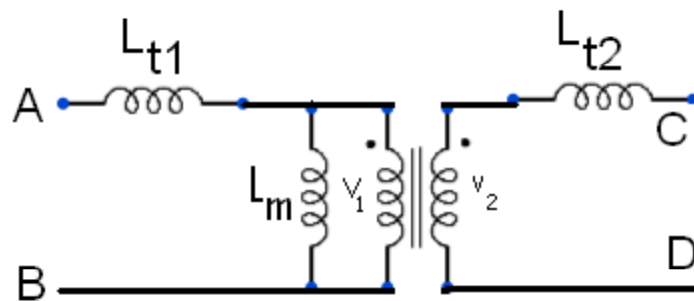- In switched mode dc-dc converters, it is desirable to minimize the leakage inductances L_{t1} and L_{t2} by providing a tight magnetic coupling between the two windings
- It is also desirable to have high “ L_m ” to minimize the magnetizing current i_m that flows through the switches and thus increases their current ratings.






Flyback Converter

- If inductor core can accommodate two coils, one winding can be used to inject energy into the inductor, while the other can be used to transfer the energy to load.
- It is also possible that these two windings need not share direct electrical connection and hence can provide isolation.
- With only one winding, the current and flux are proportional, while with two or more windings, the flux is proportional to total ampere turn of all the windings.
- Flyback converter is functionally identical to buck-boost converter, but the output polarity is positive.

Flyback Converter

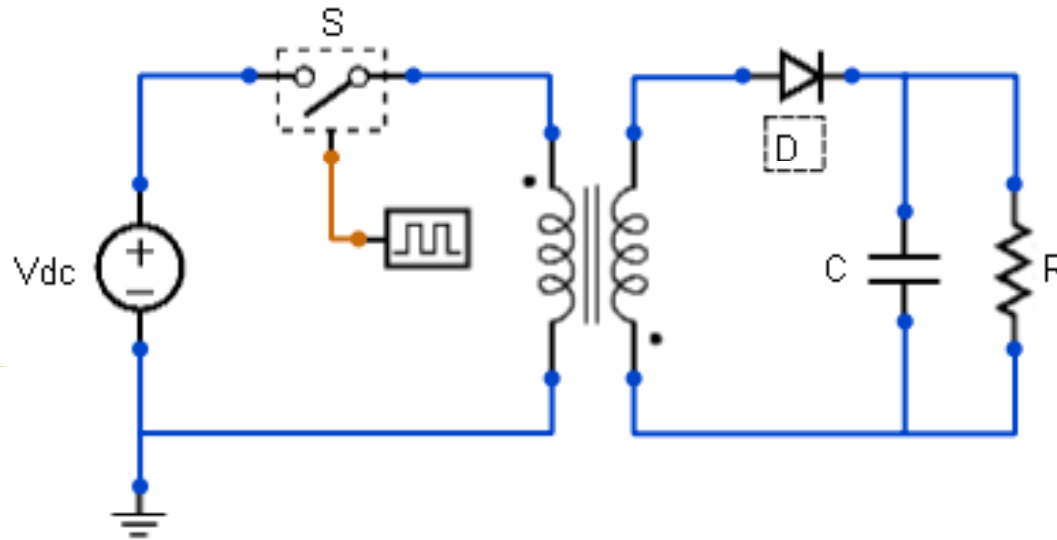

- Switch in ON State
 - Diode (D) is reverse biased

$$V_1 = V_d$$

$$\phi(t) = \phi(0) + \frac{V_d}{N_1} t$$

$$\phi(t_{on}) = \phi(0) + \frac{V_d}{N_1} t_{on}$$

Flyback Converter


- Switch is in OFF State
 - The energy stored in the core causes the current to flow in the secondary winding through the diode “D”
 - Flux decreases linearly during t_{off}

$$\left. \begin{aligned} \phi(t) &= \hat{\phi} + \frac{V_0}{N_2} (t - t_{\text{on}}) \\ \phi(T_s) &= \hat{\phi} + \frac{V_0}{N_1} (T_s - t_{\text{on}}) \end{aligned} \right\} \phi(T_s) = \phi(0) + \frac{V_d}{N_1} t_{\text{on}} - \frac{V_0}{N_2} (T_s - t_{\text{on}})$$

- At steady state: $\phi(T_s) = \phi(0)$, as net change of flux through the core over one time period must be zero

$$\frac{V_d}{N_1} t_{\text{on}} = \frac{V_0}{N_2} (T_s - t_{\text{on}}) \Rightarrow \frac{V_0}{V_d} = \frac{N_2}{N_1} \times \frac{D}{1-D}$$

Forward Converter

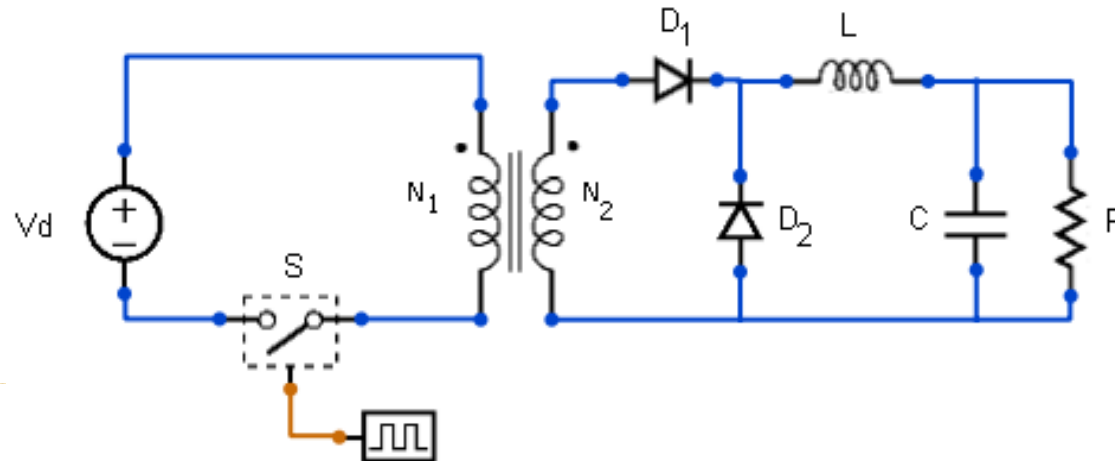

- When “S” is ON, D_1 is forward biased and D_2 is reverse biased.

$$V_L = \frac{N_2}{N_1} V_d - V_0 \quad 0 < t < t_{on}$$

- When “S” is OFF, D_1 is reverse biased and D_2 is forward.

$$V_L = -V_0 \quad t_{on} < t < T_s$$

- Equating the integral of the inductor voltage over one time period to zero gives:

$$\frac{V_0}{V_d} = \frac{N_2}{N_1} D$$

dc-dc Converters

- **COMPARISON OF CONVERTERS**

Converter	Output voltage	Boundary Condition
Buck	$V_o = DV_d$	$I_{LB} = \frac{T_s V_d}{2L} D(1-D)$
Boost	$V_o = \frac{1}{1-D} V_d$	$I_{OB} = \frac{T_s V_o}{2L} D(1-D)^2$
Buck-Boost	$V_o = \frac{D}{1-D} V_d$	$I_{OB} = \frac{T_s V_o}{2L} (1-D)^2$
Cuk	$V_o = \frac{D}{1-D} V_d$	
Full bridge converter	$V_o = \frac{V_d}{\hat{V}_{tri}} V_{control}$	<ul style="list-style-type: none">• Uni-polar• Bi-polar