

EN 206 1/30

## EN 206 - Power Electronics and Machines Synchronous Machine

Suryanarayana Doolla Department of Energy Science and Engineering Indian Institute of Technology, Bombay suryad@iitb.ac.in

▲ロト ▲帰ト ▲ヨト ▲ヨト 三日 - の々ぐ



## Lecture Organization - Modules

EN 206 2/30

- Introduction and Power Semiconductor Switches
- Module 1: Transformers
- Module 2: AC/DC converter / Rectifier
- Module 3: DC machines and Drives
- Module 4: DC/DC converter
- Module 5: Induction Machine
- Module 6: DC/AC converter / Inverter
- Module 7: AC/AC converter / Cyclo converter
- Module 8: Synchronous Machine
- Module 9: Special Topics: Machines, HVDC, APF



#### Construction

EN 206 3/30

- Synchronous Motor/Generator
  - Field is rotating (large size machines)
  - Armature is stationary

#### Rotor

- Salient pole (Low Speed- Hydro turbine)
- Non-Salient pole (High Speed Steam turbine)
- Field is excited by 'dc' supply
  - DC generator
  - Power Electronic converter
  - Brush less excitation
- AC voltage is available across armature/stationary conductors

- Concentrated winding
- Distributed winding



# EMF Generation in Synchronous Machine

EN 206 4/30



- Assume : The poles are moving to left, then relative motion of conductors is to the right
- Identical magnetic conditions will be seen by coil A followed by C and followed by B.
- Induces EMF with phase sequence of ACB



EN 206 5/30

# Frequency in Synchronous Generator



#### In one revolution

- **1** Two pole machine generates one full waveform (one cycle)
- 2 Four pole machine generates two full waveforms (two cycles)
- Electrical degrees = pole pair \* mechanical degree of rotation
- For one revolution/sec, the frequency of emf wave = pole pair

・ロン ・ 理 と ・ ヨ と ・ ヨ ・ うへつ

Frequency = (P/2)\*(N/60)=(PN)/120



## Construction - Generator

EN 206 6/30

- Salient Pole Rotor
  - 4 pole, three phase salient pole rotor with concentric field windings.





## Connections - Generator

EN 206 7/30

- Distributed armature winding
  - Three phase armature winding is distributed in 12 slots 4 slots per pole.





## Rotor Structures

EN 206 8/30





## Rotor MMF

EN 206 9/30 Prof. Doolla

Cylindrical rotor mmf wave and its fundamental of a synchronous machine



◆□▶ ◆□▶ ◆三▶ ◆三▶ 三三 のへぐ



#### Excitation Systems

EN 206 10/30

- Field ac or dc?
- Adjustment of field current can be either automatic or manual based on complexity of system it is connected to.
- Voltage is up to 125V for 50kW system and higher voltage for higher system rating.





## Loaded Generator - UPF

EN 206 11/30



- Assume: A conductor induces maximum emf when it is under direct influence of pole.
- Current and emf magnitude are maximum at same instant in case of purely resistive loads.
- The flux produced by the armature is demagnetizing under north pole and magnetizing under south pole.
- The next flux remains same in the airgap



# Loaded Generator - ZPF (lagging)

EN 206 12/30



- Assume: A conductor induces maximum emf when it is under direct influence of pole.
- Current is maximum when voltage is minimum.
- The flux produced by the armature is demagnetizing under both north pole and south pole.
- The next flux in the airgap reduces.



# Loaded Generator - ZPF (leading)

EN 206 13/30



- Assume: A conductor induces maximum emf when it is under direct influence of pole.
- Current is maximum when voltage is minimum.
- The flux produced by the armature is magnetizing under both north pole and south pole.
- The next flux in the airgap increases.



## Armature and Field mmf

EN 206 14/30

Prof. Doolla

- If I<sub>a</sub> lags emf by 90<sup>0</sup> (zero power factor) then it can be proven the F<sub>a</sub> is entirely demagnetizing F<sub>f</sub>.
- If *I<sub>a</sub>* leads emf by 90<sup>0</sup> (zero power factor) then it can be proven the *F<sub>a</sub>* is entirely magnetizing *F<sub>f</sub>*.
- For motoring operation the same analysis is applicable by substituting *I<sub>a</sub>* in place of *I<sub>a</sub>*
- If armature current lags emf by 90<sup>0</sup>, the nature of armature mmf is
  - demagnetizing in an alternator
  - magnetizing in a synchronous motor
- If armature current leads emf by 90<sup>0</sup>, the nature of armature mmf is
  - magnetizing in an alternator
  - demagnetizing in a synchronous motor



# Phasor Diagram-Resistive and inductive load





EN 206 16/30

Prof. Doolla

- Open circuit and short circuit characteristics are useful to determine the parameters of a synchronous machine
- OCC: The alternator is driven at rated speed and open circuit voltage reading is noted as the field current is increased. The final value of *E<sub>f</sub>* should be 125% of the rated voltage
- OCC is also called as no-load, saturation or magnetization characteristic and is not straight line because of saturation in the iron part of magnetic circuit.
- SCC: The machine is driven at rated synchronous speed and the armature terminals are short-circuited through an ammeter. The field current is varied till the armature current reading is 125 to 150% of rated value.
- SCC is a straight line through origin. Saturation does not occur as F<sub>a</sub> is demagnetizing in nature



# Characteristics of Synchronous Generator





# Voltage Regulation of Synchronous Generator

EN 206 18/30

Prof. Doolla

- It is defined as change in terminal voltage expressed as a percentage of the rated voltage, when the load at a given power factor is removed.
- In case of small machines, this test can be directly performed
- In case of large machines, it is not economical or technically feasible to perform voltage regulation test at laboratory
- Voltage regulation helps in
  - determining the voltage levels insulation level
  - Automatic voltage regulator equipment design
  - Steady state short-circuit condition and stability are effected by the voltage regulation
  - Parallel operation of one alternator with other alternator, is effected considerable by voltage regulation



# Methods - Determine Voltage Regulation

EN 206 19/30

Prof. Doolla

- EMF method or synchronous impedance method (Pessimistic approach)
  - Applicable for cylindrical rotor machines
  - The lowest values of Z<sub>s</sub> obtained from largest value of SCC is used in computation
  - SCC: The effect of armature flux is demagnetizing and hence the flux density is much less than the flux density in actual condition - an unsaturated value of Z<sub>s</sub> is obtained.

- Mmf method (Optimistic Approach)
- ZPF method (Potier traingle)
- New ASA method
- Saturated synchronous reactance method



# EMF Method - Cylindrical rotor

EN 206 20/30

Prof. Doolla

Field mmf  $F_f$  generates  $E_f$  lagging it by 90<sup>0</sup>

- Resultant mmf F<sub>r</sub> generates E<sub>r</sub> lagging it by 90<sup>0</sup>. Armature reaction mmf F<sub>r</sub> generates E<sub>ar</sub> lagging it by 90<sup>0</sup>
- X<sub>ar</sub> is armature reaction reactance, it is a fictitious reactance which accounts for the voltage E<sub>ar</sub> generated by armature reaction mmf E<sub>a</sub>.
- The term r<sub>a</sub> + jX<sub>s</sub> = Z<sub>s</sub> is called synchronous impedance, X<sub>s</sub> = X<sub>al</sub> + X<sub>ar</sub>





EN 206 21/30

The analysis of synchronous machine can be carried out by using phasor diagram For an alternator, phasor  $E_f$  is always ahead of phasor  $V_t$ , and

for a synchronous motor, phasor  $E_f$  is always behind phasor  $V_t$ 



イロト 不得 トイヨト イヨト 三日



### Power flow between two nodes

EN 206 22/30

Prof. Doolla

For a cylindrical rotor machine Generator

 $P_{ig} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{E_f^2}{Z_s^2} r_a$  $P_{og} = \frac{E_f V_t}{Z_s} sin(\delta + \alpha_z) - \frac{V_t^2}{Z_s^2} r_a$ 

• 
$$Q_{og} = \frac{E_f V_t}{Z_s} cos(\delta + \alpha_z) - \frac{V_t^2}{Z_s^2} X_s$$

Motor

 $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} r_a$  $P_{om} = \frac{E_f V_t}{Z_s} sin(\delta + \alpha_z) - \frac{E_f^2}{Z_s^2} r_a$  $Q_{im} = -\frac{E_f V_t}{Z_s} cos(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} X_s$ 



◆□▶ ◆□▶ ◆臣▶ ◆臣▶ ─臣 ─ のへで



EN 206 23/30

> A synchronous machine has been synchronized with an infinite bus. Now, without changing the field current, the machine is made to deliver real power to the bus. Will it, at the same time, generate or consume reactive power?

> > ▲ロト ▲帰ト ▲ヨト ▲ヨト 三日 - の々ぐ



EN 206 23/30

> A synchronous machine has been synchronized with an infinite bus. Now, without changing the field current, the machine is made to deliver real power to the bus. Will it, at the same time, generate or consume reactive power?

For proper synchronization,  $V_t = E_f$ , therefore, reactive power  $Q = \frac{V_t^2}{X_s} (\cos \delta - 1)$ .



EN 206 23/30

> A synchronous machine has been synchronized with an infinite bus. Now, without changing the field current, the machine is made to deliver real power to the bus. Will it, at the same time, generate or consume reactive power?

- For proper synchronization,  $V_t = E_f$ , therefore, reactive power  $Q = \frac{V_t^2}{X_s} (\cos \delta 1)$ .
- As the motor is supplying active power  $\delta \neq 0$  and also  $cos\delta < 1$ , therefore Q is negative.



EN 206 23/30

> A synchronous machine has been synchronized with an infinite bus. Now, without changing the field current, the machine is made to deliver real power to the bus. Will it, at the same time, generate or consume reactive power?

- For proper synchronization,  $V_t = E_f$ , therefore, reactive power  $Q = \frac{V_t^2}{X_s} (\cos \delta 1)$ .
- As the motor is supplying active power  $\delta \neq 0$  and also  $cos\delta < 1$ , therefore Q is negative.
- Q is negative, indicates that the generator is absorbing reactive power.

(日) (同) (三) (三) (三) (○) (○)



EN 206 23/30

> A synchronous machine has been synchronized with an infinite bus. Now, without changing the field current, the machine is made to deliver real power to the bus. Will it, at the same time, generate or consume reactive power?

- For proper synchronization,  $V_t = E_f$ , therefore, reactive power  $Q = \frac{V_t^2}{X_s} (\cos \delta 1)$ .
- As the motor is supplying active power  $\delta \neq 0$  and also  $cos\delta < 1$ , therefore Q is negative.
- Q is negative, indicates that the generator is absorbing reactive power.

(日) (同) (三) (三) (三) (○) (○)



EN 206 24/30

A synchronous generator is running overexcited with  $E_F = 1.40 pu$ . This machine, with a synchronous reactance of 1.20pu is delivering a synchronous power of 0.5pu to the bus. If the primemover torque is increased by 1%, by how much will the active power P and reactive power Q change?



EN 206 24/30

A synchronous generator is running overexcited with  $E_F = 1.40 pu$ . This machine, with a synchronous reactance of 1.20pu is delivering a synchronous power of 0.5pu to the bus. If the primemover torque is increased by 1%, by how much will the active power P and reactive power Q change?

$$P = \frac{E_f V_t}{X_s} \sin \delta, \rightarrow 0.5 = \frac{1.4 \times 1}{1.2} \sin \delta \rightarrow \delta = 25.4^{\circ}$$



EN 206 24/30

A synchronous generator is running overexcited with  $E_F = 1.40 pu$ . This machine, with a synchronous reactance of 1.20pu is delivering a synchronous power of 0.5pu to the bus. If the primemover torque is increased by 1%, by how much will the active power P and reactive power Q change?

$$P = \frac{E_f V_t}{X_s} \sin \delta, \rightarrow 0.5 = \frac{1.4 \times 1}{1.2} \sin \delta \rightarrow \delta = 25.4^{\circ}$$

 1% increase in torque means 1% increase in real power (speed is constant), therefore dP=1% of its previous value.



EN 206 24/30

A synchronous generator is running overexcited with  $E_F = 1.40 pu$ . This machine, with a synchronous reactance of 1.20pu is delivering a synchronous power of 0.5pu to the bus. If the primemover torque is increased by 1%, by how much will the active power P and reactive power Q change?

$$P = \frac{E_f V_t}{X_s} \sin \delta, \rightarrow 0.5 = \frac{1.4 \times 1}{1.2} \sin \delta \rightarrow \delta = 25.4^{\circ}$$

 1% increase in torque means 1% increase in real power (speed is constant), therefore dP=1% of its previous value.

$$Q = \frac{E_f V_t}{X_s} \cos \delta - \frac{V_t^2}{X_s} \rightarrow \frac{dQ}{d\delta} = -\frac{E_f V_t}{X_s} \sin \delta$$



EN 206 24/30

A synchronous generator is running overexcited with  $E_F = 1.40 pu$ . This machine, with a synchronous reactance of 1.20pu is delivering a synchronous power of 0.5pu to the bus. If the primemover torque is increased by 1%, by how much will the active power P and reactive power Q change?

$$P = \frac{E_f V_t}{X_s} \sin \delta, \rightarrow 0.5 = \frac{1.4 \times 1}{1.2} \sin \delta \rightarrow \delta = 25.4^{\circ}$$

 1% increase in torque means 1% increase in real power (speed is constant), therefore dP=1% of its previous value.

$$Q = \frac{E_f V_t}{X_s} \cos \delta - \frac{V_t^2}{X_s} \rightarrow \frac{dQ}{d\delta} = -\frac{E_f V_t}{X_s} \sin \delta$$

■  $\frac{dQ}{dP} = -tan\delta = tan(25.4) = -0.475$ , therefore  $dQ=-0.475 \times 1\% = -0.475\%$ 



EN 206 24/30

A synchronous generator is running overexcited with  $E_F = 1.40 pu$ . This machine, with a synchronous reactance of 1.20pu is delivering a synchronous power of 0.5pu to the bus. If the primemover torque is increased by 1%, by how much will the active power P and reactive power Q change?

$$P = \frac{E_f V_t}{X_s} \sin \delta, \rightarrow 0.5 = \frac{1.4 \times 1}{1.2} \sin \delta \rightarrow \delta = 25.4^{\circ}$$

 1% increase in torque means 1% increase in real power (speed is constant), therefore dP=1% of its previous value.

$$Q = \frac{E_f V_t}{X_s} \cos \delta - \frac{V_t^2}{X_s} \rightarrow \frac{dQ}{d\delta} = -\frac{E_f V_t}{X_s} \sin \delta$$

■  $\frac{dQ}{dP} = -tan\delta = tan(25.4) = -0.475$ , therefore  $dQ=-0.475 \times 1\% = -0.475\%$ 

"1% increase in primemover torque leads to 1% increase in real power but 0.475% decrease in reactive power."



#### Reactive Power Flow

EN 206 25/30

Generator

- When E<sub>f</sub> cosδ > V<sub>t</sub> (over excited), Q<sub>og</sub> is positive and delivers reactive power, alternator operates at lagging pf
- When  $E_f cos \delta = V_t$  (normal excited),  $Q_{og}$  is zero and alternator operates at unity pf
- When E<sub>f</sub> cos δ < V<sub>t</sub> (under excited), Q<sub>og</sub> is negative and absorbs reactive power, alternator operates at leading pf Motor
  - When E<sub>f</sub> cos δ > V<sub>t</sub> (over excited), Q<sub>im</sub> is negative and delivers reactive power, motor operates at leading pf
  - When  $E_f cos \delta = V_t$  (normal excited),  $Q_{im}$  is zero and alternator operates at unity pf
  - When  $E_f cos \delta < V_t$  (under excited),  $Q_{im}$  is positive and absorbs reactive power, motor operates at lagging pf





EN 206 26/30

Prof. Doolla

A 3300V, star connected synchronous motor has synchronous impedance of 0.4+j0.5 ohm/phase. For an excitation emf of 4000V and motor input power of 1000kW at rated voltage, compute the line current and power factor.



EN 206 27/30

Given Data:  

$$V_t = 3300/\sqrt{3} = 1905.3V, \alpha_z = tan^{-1}(0.4/5) = 4.57^{\circ},$$
  
 $E_f = 4000/\sqrt{3} = 2309.5V, Z_s = \sqrt{0.4^2 + 5^2} = 5.016$   
Input power (per phase) for the machine is given by  
 $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} r_a$ , substituting

◆□▶ ◆□▶ ◆臣▶ ◆臣▶ 臣 のへぐ



EN 206 27/30

Given Data:  

$$V_t = 3300/\sqrt{3} = 1905.3V, \alpha_z = tan^{-1}(0.4/5) = 4.57^\circ,$$
  
 $E_f = 4000/\sqrt{3} = 2309.5V, Z_s = \sqrt{0.4^2 + 5^2} = 5.016$   
Input power (per phase) for the machine is given by  
 $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} r_a,$  substituting  
 $1000000/3 = \frac{1905.3\times2309.5}{5.016} sin(\delta - \alpha_z) + \frac{1905.3^2}{5.016^2} \times 0.4$ 

◆□▶ ◆□▶ ◆臣▶ ◆臣▶ 臣 のへぐ



EN 206 27/30 Given Data:  $V_t = 3300/\sqrt{3} = 1905.3V, \alpha_z = tan^{-1}(0.4/5) = 4.57^\circ,$   $E_f = 4000/\sqrt{3} = 2309.5V, Z_s = \sqrt{0.4^2 + 5^2} = 5.016$ Input power (per phase) for the machine is given by  $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} r_a,$  substituting  $1000000/3 = \frac{1905.3\times2309.5}{5.016} sin(\delta - \alpha_z) + \frac{1905.3^2}{5.016^2} \times 0.4$  $sin(\delta - \alpha_z) = 0.314, \delta = 18.31 + 4.57 = 22.88^\circ$ 



EN 206 27/30 Given Data:  $V_t = 3300/\sqrt{3} = 1905.3V, \alpha_z = tan^{-1}(0.4/5) = 4.57^{\circ},$   $E_f = 4000/\sqrt{3} = 2309.5V, Z_s = \sqrt{0.4^2 + 5^2} = 5.016$ Input power (per phase) for the machine is given by  $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} r_a,$  substituting  $1000000/3 = \frac{1905.3\times2309.5}{5.016} sin(\delta - \alpha_z) + \frac{1905.3^2}{5.016^2} \times 0.4$   $sin(\delta - \alpha_z) = 0.314, \delta = 18.31 + 4.57 = 22.88^{\circ}$ From the vector diagram

$$I_a Z_s = \sqrt{1905.3^2 + 2309.5.3^2 - 2x1905.3x2309.5xcos(22.88)}$$



EN 206 27/30 Given Data:  $V_t = 3300/\sqrt{3} = 1905.3V, \alpha_z = tan^{-1}(0.4/5) = 4.57^\circ,$   $E_f = 4000/\sqrt{3} = 2309.5V, Z_s = \sqrt{0.4^2 + 5^2} = 5.016$ Input power (per phase) for the machine is given by  $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} r_a,$  substituting  $1000000/3 = \frac{1905.3\times2309.5}{5.016} sin(\delta - \alpha_z) + \frac{1905.3^2}{5.016^2} \times 0.4$   $sin(\delta - \alpha_z) = 0.314, \delta = 18.31 + 4.57 = 22.88^\circ$ From the vector diagram

$$\sqrt{1905.3^2 + 2309.5.3^2 - 2x1905.3x2309.5xcos(22.88)}$$

$$I_a = 184.43A$$



EN 206 27/30 Given Data:  $V_t = 3300/\sqrt{3} = 1905.3V, \alpha_z = tan^{-1}(0.4/5) = 4.57^{\circ},$   $E_f = 4000/\sqrt{3} = 2309.5V, Z_s = \sqrt{0.4^2 + 5^2} = 5.016$ Input power (per phase) for the machine is given by  $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} r_a,$  substituting  $1000000/3 = \frac{1905.3 \times 2309.5}{5.016} sin(\delta - \alpha_z) + \frac{1905.3^2}{5.016^2} \times 0.4$   $sin(\delta - \alpha_z) = 0.314, \delta = 18.31 + 4.57 = 22.88^{\circ}$ From the vector diagram  $I_a Z_s =$ 

 $\sqrt{1905.3^2 + 2309.5.3^2 - 2x1905.3x2309.5xcos(22.88)}$ 

$$I_a = 184.43A$$

• 
$$3V_t I_a \cos(\theta) = 1000 kW$$



EN 206 27/30

Given Data:  $V_t = 3300/\sqrt{3} = 1905.3V, \alpha_z = tan^{-1}(0.4/5) = 4.57^{\circ},$  $E_f = 4000/\sqrt{3} = 2309.5V$ ,  $Z_s = \sqrt{0.4^2 + 5^2} = 5.016$ Input power (per phase) for the machine is given by •  $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} r_a$ , substituting •  $1000000/3 = \frac{1905.3 \times 2309.5}{5.016} \sin(\delta - \alpha_z) + \frac{1905.3^2}{5.016^2} \times 0.4$ •  $sin(\delta - \alpha_z) = 0.314, \ \delta = 18.31 + 4.57 = 22.88^{\circ}$ From the vector diagram  $I_a Z_s =$  $\sqrt{1905.3^2 + 2309.5.3^2 - 2x1905.3x2309.5xcos(22.88)}$ 

$$I_a = 184.43A$$

• 
$$3V_t I_a \cos(\theta) = 1000 kW$$
  
•  $\cos\theta = \frac{1000000}{3 \times 1905.3 \times 184.43} = 0.9486$ 



EN 206 27/30

Given Data:  $V_t = 3300/\sqrt{3} = 1905.3V, \alpha_z = tan^{-1}(0.4/5) = 4.57^{\circ},$  $E_f = 4000/\sqrt{3} = 2309.5V$ ,  $Z_s = \sqrt{0.4^2 + 5^2} = 5.016$ Input power (per phase) for the machine is given by •  $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_z^2} r_a$ , substituting •  $1000000/3 = \frac{1905.3 \times 2309.5}{5.016} sin(\delta - \alpha_z) + \frac{1905.3^2}{5.016^2} \times 0.4$ •  $sin(\delta - \alpha_z) = 0.314, \ \delta = 18.31 + 4.57 = 22.88^{\circ}$ From the vector diagram  $I_a Z_s =$  $\sqrt{1905.3^2 + 2309.5.3^2 - 2x1905.3x2309.5xcos(22.88)}$  $I_a = 184.43A$ •  $3V_t I_a \cos(\theta) = 1000 kW$ 

•  $cos\theta = \frac{1000000}{3 \times 1905.3 \times 184.43} = 0.9486$ •  $E_f cos\delta = 2309.5 \times cos(22.88) = 2127.87 > 1905.3$ 



EN 206 27/30

Given Data:  

$$V_t = 3300/\sqrt{3} = 1905.3V, \alpha_z = tan^{-1}(0.4/5) = 4.57^\circ,$$
  
 $E_f = 4000/\sqrt{3} = 2309.5V, Z_s = \sqrt{0.4^2 + 5^2} = 5.016$   
Input power (per phase) for the machine is given by  
 $P_{im} = \frac{E_f V_t}{Z_s} sin(\delta - \alpha_z) + \frac{V_t^2}{Z_s^2} r_a,$  substituting  
 $1000000/3 = \frac{1905.3 \times 2309.5}{5.016} sin(\delta - \alpha_z) + \frac{1905.3^2}{5.016^2} \times 0.4$   
 $sin(\delta - \alpha_z) = 0.314, \delta = 18.31 + 4.57 = 22.88^\circ$   
From the vector diagram  
 $I_a Z_s = \sqrt{1905.3^2 + 2309.5.3^2 - 2 \times 1905.3 \times 2309.5 \times cos(22.88)}$   
 $I_a = 184.43A$   
 $3V_t I_a cos(\theta) = 1000 kW$   
 $cos\theta = \frac{1000000}{3 \times 1905.3 \times 184.43} = 0.9486$ 

•  $E_f \cos \delta = 2309.5 x \cos(22.88) = 2127.87 > 1905.3$ 

The motor is operating at a leading power factor of 0.9486.



# Synchronous machine connected to infinite bus Cylindrical rotor machine

Cylindrical rotor machine

EN 206 28/30



 Resistance of synchronous machine is usually small and hence neglected

▲ロト ▲帰ト ▲ヨト ▲ヨト 三日 - の々ぐ

- Power delivered to infinite bus  $(P) = V_t I_a cos \theta$
- From figure,  $I_a X_s \cos\theta = E_f \sin\delta$  $P_a = \frac{E_f V_t}{E_f V_t} \sin\delta$

$$P = \frac{E_f V_t}{X_s} sin\delta$$



# Synchronous machine connected to infinite bus Salient pole machine





Synchronous machine connected to infinite bus Salient pole machine

EN 206 30/30

The per phase power transferred to the bus is given by:

$$P = \frac{E_f V_t}{X_d} \sin\delta + \frac{V_t^2}{2} (\frac{1}{X_d} - \frac{1}{X_d}) \sin 2\delta$$

- It is a combination of fundamental component and second harmonic component
- The first term (identical to cylindrical rotor machine) is termed as electromagnetic power
- The armature reaction flux passes through low reluctance path (i.e., field pole axis or direct axis)
- The second component is mainly due to reluctance of both d and q axes and hence termed as reluctance power.
- Motor may continue to rotate as reluctance motor even when field excitation is reduced to zero.