

EN 206 1/19 Prof. Dooll

Introduction

Phasor Diagram Eql Ckt

OC & SC Test

EN 206 - Power Electronics and Machines Transformers

Suryanarayana Doolla Department of Energy Science and Engineering Indian Institute of Technology, Bombay suryad@iitb.ac.in



Lecture Organization - Modules

EN 206 2/19

Prof. Doolla

Introduction

Phasor Diagram Eql Ckt

- Introduction and Power Semiconductor Switches
- Module 1: Transformers
- Module 2: AC/DC converter / Rectifier
- Module 3: DC machines and Drives
- Module 4: DC/DC converter
- Module 5: Induction Machine
- Module 6: DC/AC converter / Inverter
- Module 7: AC/AC converter / Cyclo converter
- Module 8: Synchronous Machine
- Module 9: Special Topics: Machines, HVDC, APF



Review of Last Class

EN 206 3/19

Introduction

Phasor Diagram Eql Ckt

Transformers

- Types, applications, construction
- Principle of operation, emf equation
- Phasor diagram for ideal transformer and no load condition, impedance transformation



Phasor Diagram - No Load

Øm



- α: Hysteresis angle, *I_e*: exciting current, *I_φ* : Magnetizing current, *I_c*: Core loss component
- r₁: primary resistance
- x₁: fictituous quantity introduced to represent the leakage flux in primary
- Primary leakage impedance drop is about 2 to 5% even at full load.
- The magnetizing current is typically 1% of full load current and hence is neglected.



EN 206

Phasor Diagram - Lagging Load



Eql Ckt OC & SC Te



- θ₁ and θ₂ is the power factor of the load and source respectively.
- r₁: primary resistance
- x₁: fictituous quantity introduced to represent the leakage flux in primary
- Primary leakage impedance drop is about 2 to 5% even at full load.
- Phasor diagram is helpful only:
 - When a transformer is to be studied alone
 - When the internal behaviour of the transformer is to be understood



Equivalent Circuit

EN 206 6/19 Prof. Doolla

Introduction

Phasor Diagram

Eql Ckt

With Exciting current neglected:



Exact equivalent circuit:





Equivalent Circuit

EN 206 7/19 Prof. Doolla

Introduction

Phasor Diagram

Eql Ckt

Equivalent circuit referred to primary:





Problem-1

EN 206 8/19 Prof. Doolla

Introduction

Phasor Diagram

Eql Ckt

A 33 kVA, 2200/220V, single phase transformer has resistances and leakage reactances as follows:

 $r_1 = 2.4\Omega, r_2 = 6.0\Omega, x_1 = 0.03\Omega, x_2 = 0.07\Omega$

Subscripts 1 and 2 denote high voltage and low voltage windings respectively.

(a) Determine the total ohmic losses at full load.

(b) Calculate the voltage to be applied to the HV side in order to obtain a short circuit current of 160A in the LV side. Also find the input power for this condition.



Problem-2

EN 206 9/19 Prof. Doolla

Introduction

Phasor Diagram

Eql Ckt

A 10 kVA, 2500/250V, single phase transformer has resistances and leakage reactances as follows:

 $r_1 = 4.8\Omega$, $r_2 = 0.048\Omega$, $x_1 = 11.2\Omega$, $x_2 = 0.112\Omega$ Subscripts 1 and 2 denote high voltage and low voltage windings respectively. With primary voltage held constant at 2500V, calculate the secodnary terminal voltage, when (a) The low voltage winding is connected to a load of impedance of 5+j3.5 Ω .

(b) The transformer delivers its rated current at 0.8pf lagging on the low voltage side.



Open Circuit (OC) and Short Circuit (SC) Test

- EN 206 10/19 Prof. Doolla
- Introduction
- Phasor Diagram
- Eql Ckt
- OC & SC Test
- OC and SC test on a transformer are performed to find out:
 - The parameters of equivalent circuit
 - Voltage regulation
 - Efficiency

All these tests are performed without loading the transformer.



Open Circuit Test

EN 206 11/19 Prof. Doolla Introduction Phasor Diagram Edl Ckt

OC & SC Test

Circuit diagram for OC Test:



- 1 The meters are connected on low voltage side of the transformer
- 2 The high voltage side is kept open, and rated frequency voltage is applied to the primary using variac
- 3 At this condition, the rated flux flows into the core of the transformer.



Open Circuit Test

EN 206 12/19 Prof. Doolla

Introduction

Phasor Diagram

Eql Ckt

OC & SC Test

What do the meter(s) reading indicate?

- The ammeter indicate the excitation current of the transformer (no load current)
- As the value of *l_e* is small, the voltage drop across the leakage impedance can be negleced.
- The applied voltage can be assumed to be equal to emf induced (for all practical purpose)
- The reading of wattmeter gives core losses in the machine (neglecting copper losses).



OC Test - Analysis

EN 206 13/19 Prof. Doolla

Introduction

Phasor Diagram

OC & SC Test

Let V_1 be the voltage applied across the primary (LV) side of the transformer, I_e is the exciting current, P_c is core loss, then: $P_c = V_1 I_e \cos \theta$, \therefore no load power factor is given by: $\cos \theta_o = \frac{P_c}{V_1 I_e}$ From the phasor diagram, we can obtain that:

 $I_c = I_e \cos\theta_0$ and $I_{\phi} = \sin\theta_0$

$$\therefore R_c = rac{V_1}{I_e cos heta_o}$$
, $X_\phi = rac{V_1}{I_e sin heta_o}$



OC Test - Summary

EN 206 14/19 Prof. Doolla

Introduction

Phasor Diagram

Eql Ckt

OC & SC Test

- OC test on a transformer gives the following information
 - Core losses at rated voltage and frequency
 - The shunt branch parameters of the equivalent circuit (*R_c* and *X_φ*)
 - Turns ratio of the transformer

Note: The values of R_c and X_{ϕ} determined are to be referred to the side in which instruments are placed.



Short Circuit Test

EN 206 15/19 Prof. Doolla Introduction

Phasor Diagram Eql Ckt

OC & SC Test

Circuit diagram for SC Test:



1 The low voltage side terminals are short circuted.

- 2 The meters are connected on high voltage side of the transformer.
- Voltage is applied to the primary using variac (2 to 12% of V_{rated}).
- 4 At this condition, full load current will flow in both the windings.
- 5 Core flux is 1 to 6% of its rated value.



Short Circuit Test

EN 206 16/19 Prof. Doolla

Introduction

Phasor Diagram

Eql Ckt

OC & SC Test

What do the meter(s) reading indicate?

- The ammeter indicate full load current of HV side
- The reading of wattmeter gives copper losses in the machine at full load (neglecting core losses).
- The exciting current may be neglected to obtain a simplified equivalent circuit.



Short Circuit Test - Analysis

EN 206 17/19 Prof. Doolla

Introduction

Phasor Diagram Eql Ckt

OC & SC Test

If $r_{e,hv}$, $x_{e,hv}$ and $z_{e,hv}$ represent equivalent resistance, leakage reactance and impedance referred to hv side:

$$z_{e,hv} = \frac{V_{sc}}{I_{sc}}$$

$$r_{e,hv} = \frac{P_{sc}}{I_{sc}^2}$$

$$x_{e,hv} = \sqrt{z_{e,hv}^2 - r_{e,hv}^2}$$



Short Circuit Test - Summary

EN 206 18/19 Prof. Doolla

Introduction

Phasor Diagram

Eql Ckt

OC & SC Test

- SC test is generally performed on high voltage side
- The readings of SC test help in determining the resistance and leakage reactance of the windings.
- It is possible to determine the efficient of the transformer using SC test data and core losses.



Summary

EN 206 19/19

Prof. Doolla

ntroduction

Phasor Diagram

Eql Ckt

OC & SC Test

Transformers

- Phasor diagram of transformer (loaded)
- Equivalent Circuit
- Open Circuit and Short Circuit Test

Next Class

- Auto Transformer and Three phase Transformers
- Thank you!!

For Further Reading:

- Transformer Engineering: Design and Practice Authors: S.V. Kulkarni and S.A. Khaparde Publisher: Marcel Dekker (Taylor & Francis Group), New York, May 2004 ISBN: 0-8247-5653-3
- Electric Machinery: A. E. Fitzgerald, C. Kingsley, S. D. Umans. Publisher: TMH, New Delhi, India, 2009