

EN 206: Power Electronics and Machines

Un-Controlled Rectifiers

Suryanarayana Doolla

Department of Energy Science and Engineering
Indian Institute of Technology Bombay
email: suryad@iitb.ac.in

January 27, 2012


- ▶ Applications:
 - ▶ Front end for power supplies (old)
 - ▶ Battery chargers
- ▶ The power semi conductor devices are always forward biased due to dc supply voltage.
- ▶ Diode is best suited for this converter.
- ▶ Power factor is poor

Lecture Organization - Modules


- ▶ Introduction and Power Semiconductor Switches
- ▶ Module 1: Transformers
- ▶ Module 2: AC/DC converter / Rectifier
- ▶ Module 3: DC machines and Drives
- ▶ Module 4: DC/DC converter
- ▶ Module 5: Induction Machine
- ▶ Module 6: DC/AC converter / Inverter
- ▶ Module 7: AC/AC converter / Cyclo converter
- ▶ Module 8: Synchronous Machine
- ▶ Module 9: Special Topics: Machines, HVDC, APF

A Simple Diode Rectifier


Circuit

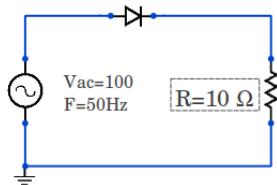


Supply Voltage and Current

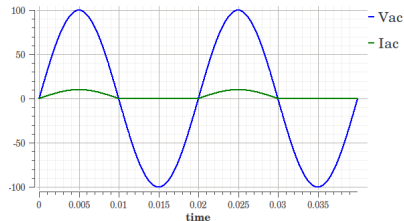

Supply and Load Voltage

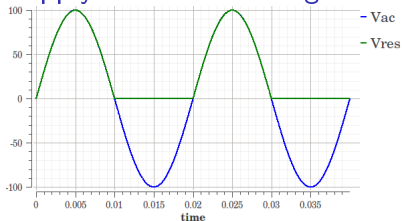

Supply and Diode Voltage

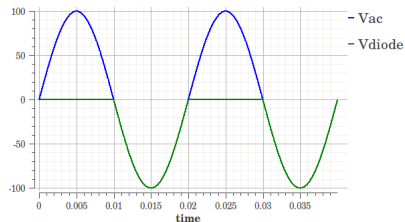

Definitions

- ▶ Average value (DC) of function, $F(t)$, is given by

$$F_{avg} = \frac{1}{T} \int_0^T f(t) dt$$

- ▶ RMS value of function, $F(t)$, is given by

$$F_{rms} = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt}$$

- ▶ Form factor, $F_{FF} = \frac{F_{rms}}{F_{avg}}$

- ▶ Ripple factor,

$$F_{ripple} = \frac{\sqrt{F_{rms}^2 - F_{avg}^2}}{F_{avg}} = \sqrt{F_{FF}^2 - 1}$$

Analysis

Average value of output voltage:

$$V_o = \frac{1}{T} \int_0^T V_m \sin(\omega t) dt = \left[-\frac{V_m}{\omega T} \cos(\omega t) \right]_0^{T/2} = \frac{V_m}{\pi}$$

RMS value of output voltage:

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V_m \sin \omega t)^2 dt} = \frac{V_m}{2}$$

Form Factor of output voltage:


$$FF = \frac{V_o}{V_{rms}} = \frac{2}{\pi}$$

Ripple Factor of output voltage:


$$RF = \sqrt{\left(\frac{2}{\pi}\right)^2 - 1}$$

Half Wave Rectifier - RL Load


Circuit

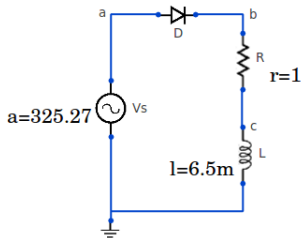

Supply voltage, load current and voltage

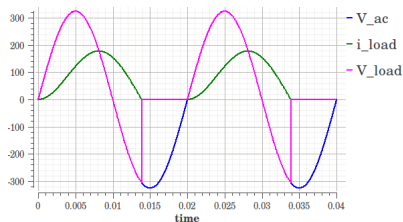

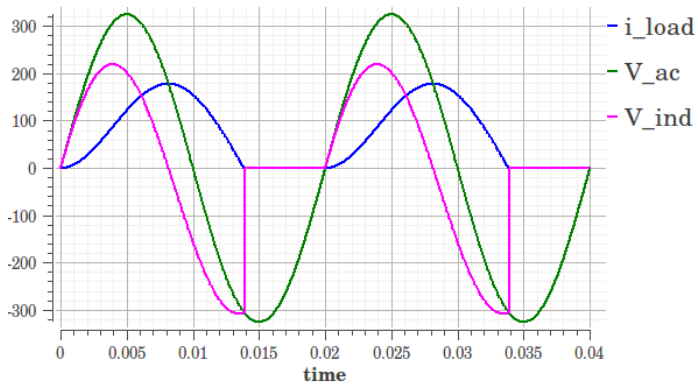- ▶ At $t=0.01\text{s}$, supply voltage moves from positive to negative half cycle.
- ▶ The load current is positive and cannot change instantaneously and hence voltage continues to follow till the inductor current becomes zero. Load voltage follows supply voltage.
- ▶ Once the load current (i_{load}) reaches zero, the diode is reverse biased and hence opens the circuit till it is forward biased.







- ▶ Because of inductive load, the current flows in the circuit even when $V_a c$ is negative.
- ▶ The total period for which the diode is conducting is termed as ' β '
- ▶ Average value of output voltage:

$$V_o = \frac{1}{2\pi} \int_0^\beta V_m \sin(\theta) d\theta = \left[-\frac{V_m}{2\pi} \cos(\theta) \right]_0^\beta = \frac{V_m}{2\pi} (1 - \cos\beta)$$

- ▶ RMS value of output voltage:

$$V_{rms} = V_m \sqrt{\frac{2\beta - \cos\beta}{2\pi}}$$



Effect of Freewheeling diode

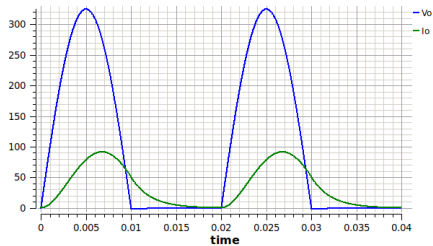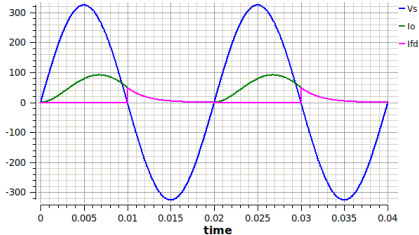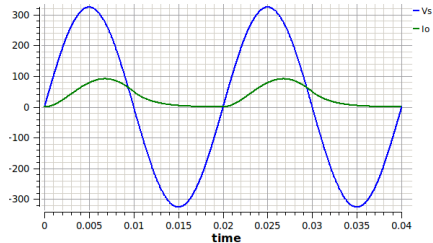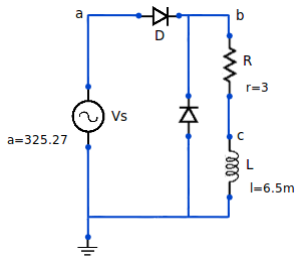

Comparison SPHWR- with R and RL Load




	R-Load	RL-Load
V_{avg}	$\frac{V_m}{\pi}$	$\frac{V_m}{\pi} \left(\frac{1 - \cos \beta}{2} \right)$
V_{rms}	$\frac{V_m}{2}$	$V_m \sqrt{\frac{2\beta - \cos \beta}{2\pi}}$
Ripple Factor	$\frac{1}{2} \sqrt{\pi^2 - 4}$	$\sqrt{\frac{\pi(2\beta - \sin 2\beta)}{2(1 - \cos \beta)^2} - 1}$

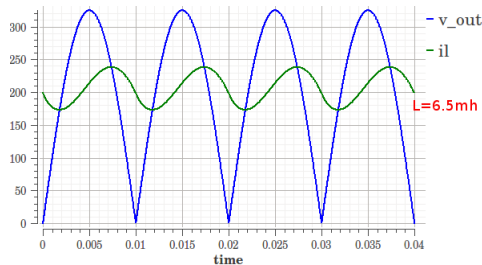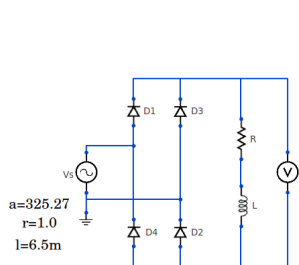Single Phase Full Bridge Rectifier -RL Load



- ▶ The output voltage is positive in both positive and negative half cycles on input supply.
- ▶ The diodes (D_1, D_2) and (D_3, D_4) conduct in pairs.
- ▶ The load current is continuous.
- ▶ By increasing the value of inductance in the load, the ripple in load current is reduced ensuring a constant dc current at the load.

Effect of inductance on supply current

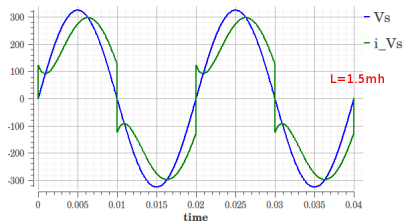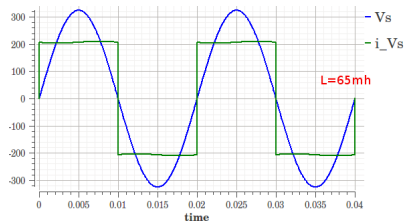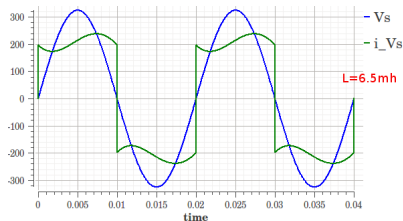

- ▶ If the load on the DC side is large (inductive), then the input current drawn by the rectifier is square wave.
- ▶ By applying fourier transform, the harmonic components of the input current waveform can be computed.

- ▶ Crest Factor, $CF = \frac{F_{peak}}{F_{rms}}$
- ▶ Distortion Factor, $DF = \frac{F_1}{F_{rms}}$
- ▶ Fundamental: It is the rms value of sinusoidal component in the waveform with frequency $1/T$.
- ▶ Harmonic: It is the rms value of sinusoidal component in the waveform with frequency K/T
- ▶ Total Harmonic Distortion (THD): It is a measure of distortion of the waveform from its fundamental
- ▶ $THD = \sqrt{\sum (\frac{F_K}{F_1})^2} = \frac{\sqrt{1-DF^2}}{DF}$

Definitions

- ▶ Displacement Factor: If ϕ_1 is the phase angle between fundamental component of voltage and current then displacement factor is given by $DPF = \cos(\phi)$
- ▶ Power factor is defined as ratio of real power to apparent power and is given by $PF = \frac{V_1 I_1 \cos \phi}{V_{rms} I_{rms}}$
- ▶ If we assume that the input voltage to the rectifier is sinusoidal, then $V_1 = V_{rms}$, therefore, $PF = \frac{I_1 \cos \phi}{I_{rms}}$,
 $PF = DPF \times DF$
- ▶ Power factor is product of displacement factor and distortion factor.
- ▶ TUF is a measure of how effectively the transformer being utilized. It is ration of average output power to product of input rms voltage and current.

Comparison HW, full wave rectifiers

Parameters	Half-wave	Full wave	
		Centre -tap	Bridge
DC output voltage	$\frac{V_m}{\pi}$	$\frac{2V_m}{\pi}$	$\frac{2V_m}{\pi}$
RMS output voltage	$\frac{V_m}{2}$	$\frac{V_m}{\sqrt{2}}$	$\frac{V_m}{\sqrt{2}}$
Ripple factor	1.211	0.482	0.482
Peak Inverse Voltage	V_m	$2V_m$	V_m
TUF	0.2865	0.672	0.8106


Three phase Rectifier

- ▶ Higher dc output voltage, better TUF
- ▶ Better input power factor
- ▶ Less ripple content in the output current hence better load performance
- ▶ Lower filter size because of high ripple frequency.

Classification:

- ▶ Three phase half wave rectifier
- ▶ Three phase mid-point 6-pulse rectifier
- ▶ Three phase bridge rectifier
- ▶ Three phase 12-pulse rectifier

Three phase Half Wave Rectifier - R Load

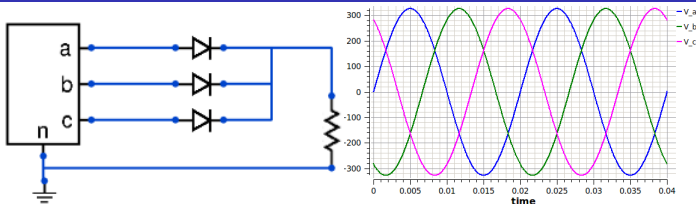

- ▶ Cathodes of three diodes are connected to the load
- ▶ The rectifier element connected to the line at the highest positive instantaneous voltage can only conduct.
- ▶ D1 conduct from $\omega t = 30^\circ$ to $\omega t = 150^\circ$ as it senses most positive voltage, D2 conduct from $\omega t = 150^\circ$ to $\omega t = 270^\circ$, D1 conduct from $\omega t = 270^\circ$ to $\omega t = 390^\circ$.


- ▶ Average output voltage $V_o = \frac{3}{2\pi} \int_{\frac{\pi}{6}}^{\frac{5\pi}{6}} V_{mp} \sin \omega t d(\omega t) = \frac{3\sqrt{3}}{2\pi} V_{mp}$

- ▶ $V_{rms} = 0.84 V_{mp}$, ripple factor=0.1826, TUF=0.6644.

Three phase diode bridge rectifier - R Load

- ▶ Upper diodes constitute the positive group diodes (D1, D3, D5)
- ▶ Lower diodes constitute the negative group diodes (D2, D4, D6)
- ▶ Positive group of diodes conduct when these have the most positive anode.
- ▶ Negative group of diodes conduct when these have the most negative anode.
- ▶ D1(30-150), D3(150-270), D5(270-390), D2(90-210), D4(210-330), D6(330-450). All angles are in degrees.

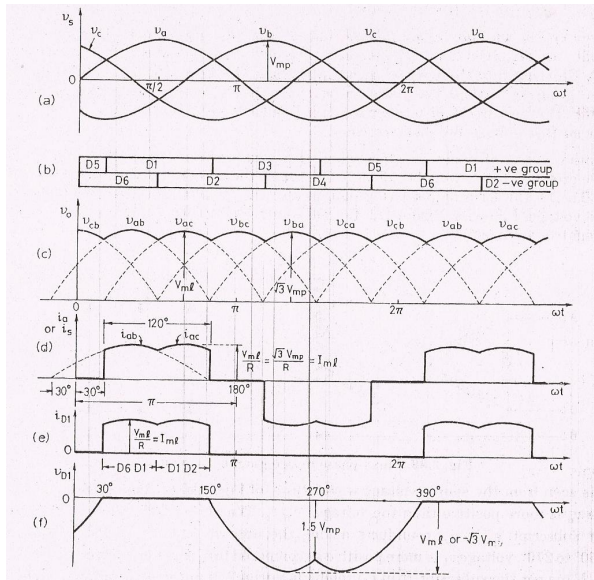
Three phase diode bridge rectifier - R Load



Three phase diode bridge rectifier - R Load


- ▶ Average o/p voltage $V_o = \frac{3}{\pi} \int_{\frac{\pi}{6}}^{\frac{\pi}{2}} V_{ml} \sin(\omega t + 30^\circ) d(\omega t) = \frac{3V_{ml}}{\pi}$
- ▶ $V_o = \frac{3V_{ml}}{\pi} = \frac{3\sqrt{2}V_{LL}}{\pi} = \frac{3\sqrt{6}V_p}{\pi}$
- ▶ $V_{rms} = 0.9558 V_{ml}$, ripple factor = 0.0427
- ▶ Transformer utilization factor (TUF) = 0.9541

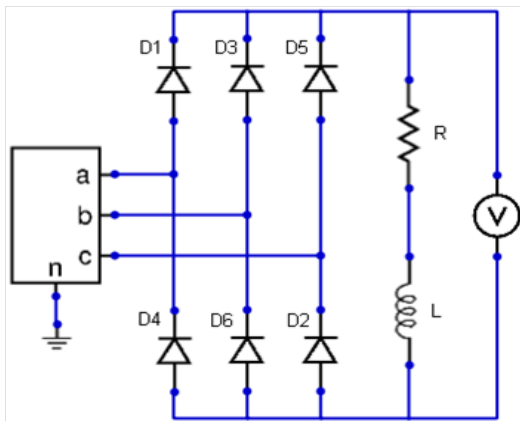Three phase Diode Bridge Rectifier - RL Load




Three phase Diode Bridge Rectifier - RL Load


Supply Voltage(Phase)

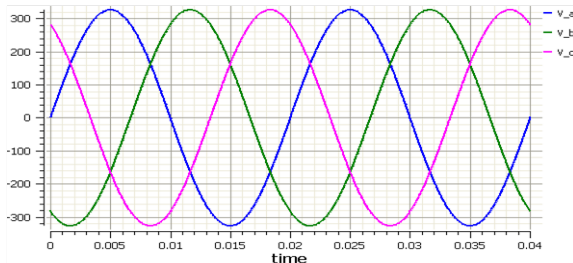


Supply Voltage(Line-Line)

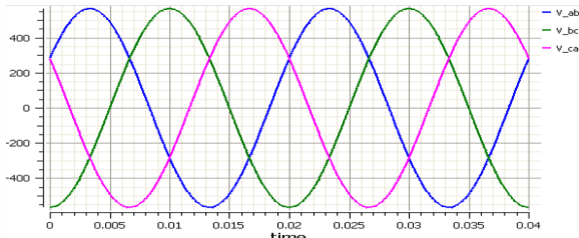

Output Voltage and Input phase voltage

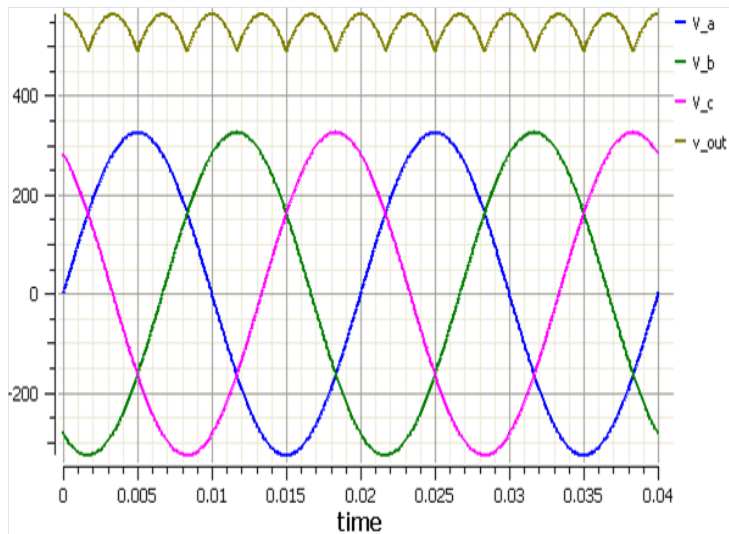


Output Voltage and Input phase voltage

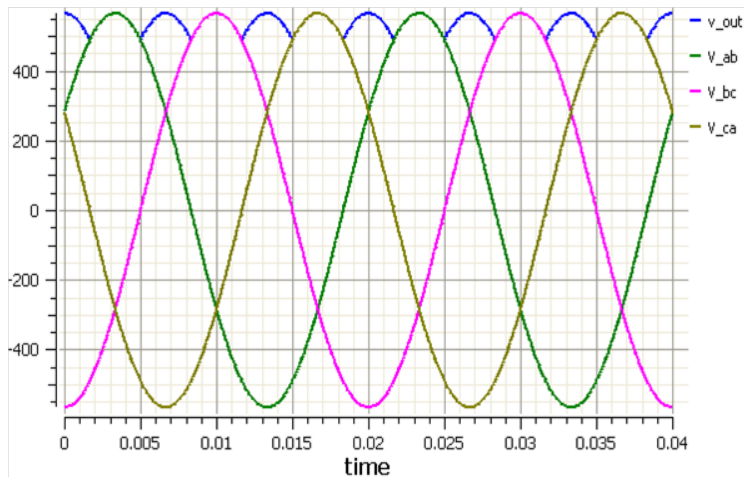


- ▶ Conduction Sequence: A(D1), B(D3), C(D5)
- ▶ AB-AC, BC-BA, CA-CB





Phase Voltage and Diode Current

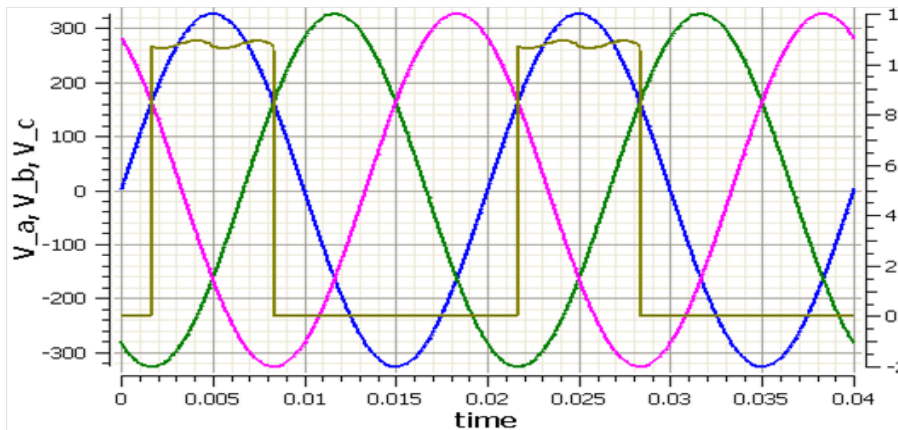


Line Voltage and Diode Current

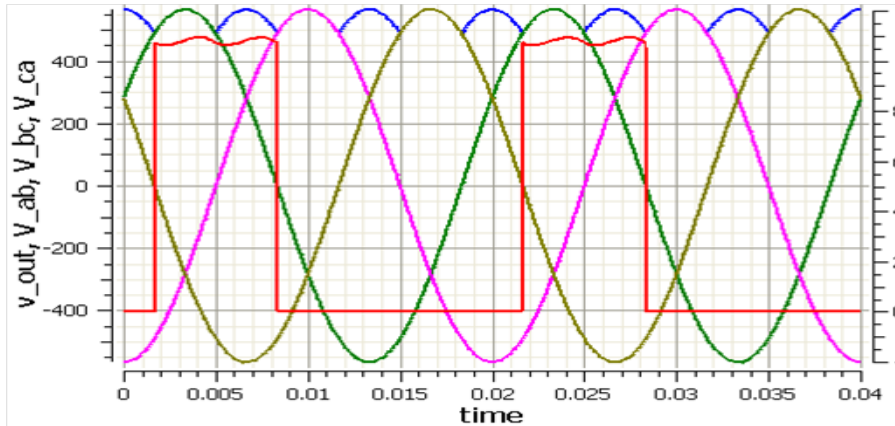

Diode and Source Current

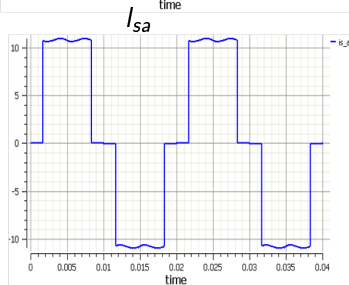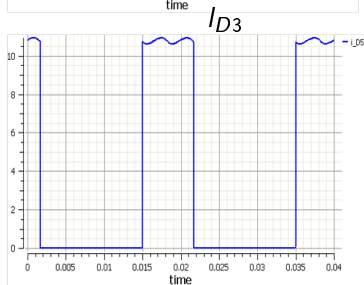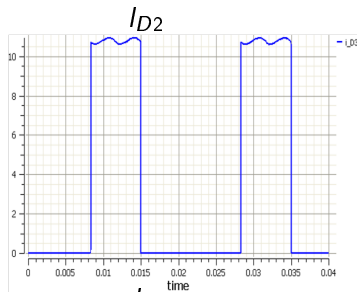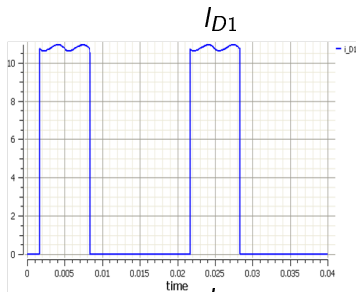


Input Voltage and Source Current

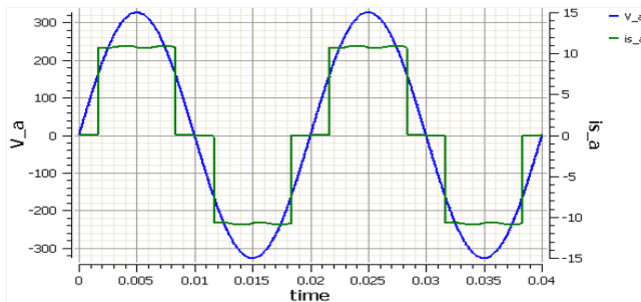

- ▶ Assume that peak current is flat in nature, $I_{rms} = I_o \sqrt{\frac{2}{3}}$
- ▶ $b_1 = \frac{2\sqrt{3}}{\pi} I_o$ (Using Fourier Transforms)
- ▶ What happens to power factor assuming the supply is pure sinusoidal?
- ▶ Distortion factor = 0.9549, Total Harmonic Distortion = 31.08%
- ▶ Power Factor = $DF \times DPF$

Classical Diode Bridge Rectifier

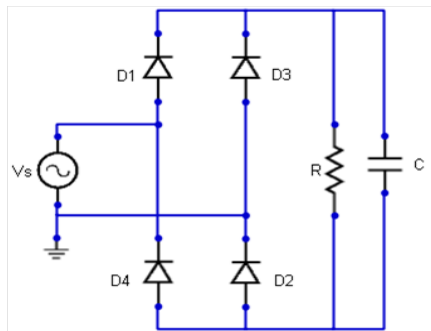


- ▶ Simplicity in circuit and hence used in most of the applications as a front end.
- ▶ Possible to have flat dc voltage but generates peaky input current
- ▶ These converters have led to poor power factor and major problem to utility (current distortion)

Classical Diode Bridge Rectifier


- ▶ When diode pair is ON, $V_{out} = |V_{in}|$.
- ▶ When the diode is OFF, V_{out} decreases exponentially depending on the time constant of RC circuit.
- ▶ Diode is OFF when $I_R + I_C = 0$, i.e., when capacitive current and resistive current balance out.
- ▶ The decay will continue as long as diodes are reverse biased, i.e., $|V_{in}| < V_{out}$
- ▶ To have low ripple, RC time constant should be much greater than the half of the input waveform period.

Classical Diode Bridge Rectifier

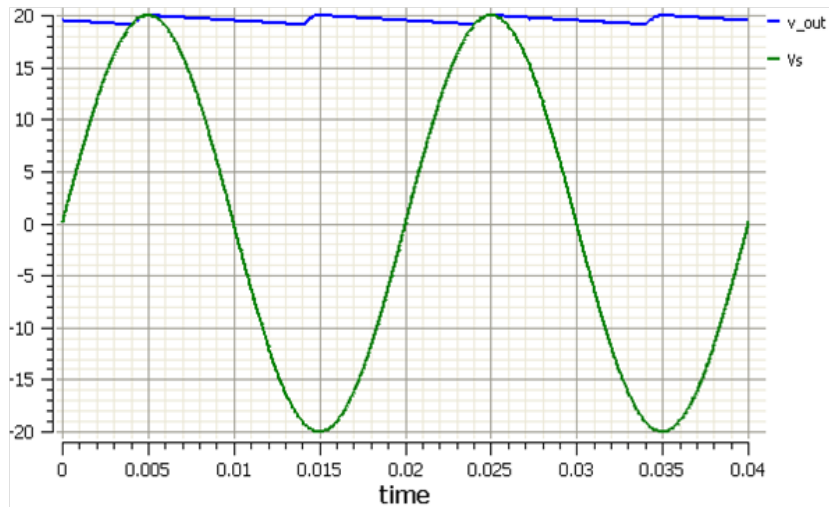System: $V_s = 20\sin(\omega t)$, $R=6$, $C=0.33000\mu\text{F}$





Classical Diode Bridge Rectifier

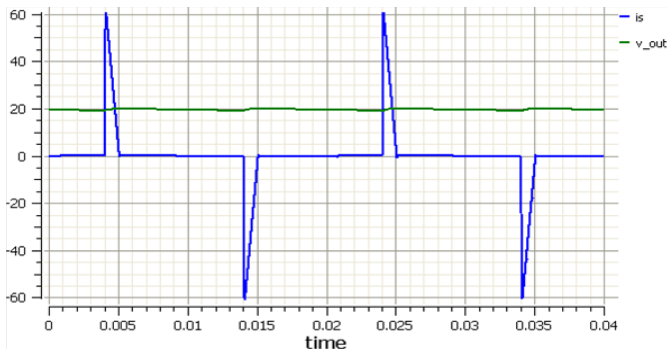

- ▶ Output is directly linked with peak of input and hence line regulation is poor. To achieve good load regulation large capacitor is required.
- ▶ Transformer provides isolation between input and output, but average value is restricted once transformer is selected.


Diode Bridge Rectifier - RC Load

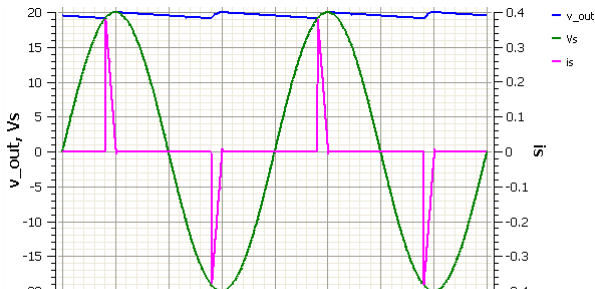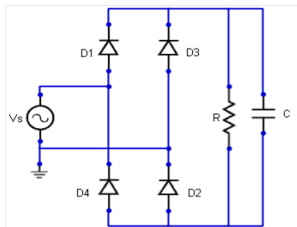$V_{s,peak} = 20$, $F=50$ Hz, $r = 1k\Omega$, $c=200\mu$, $r_{on} = 0.1m\Omega$,
 $r_{off} = 1M\Omega$



Diode Bridge Rectifier - RC Load
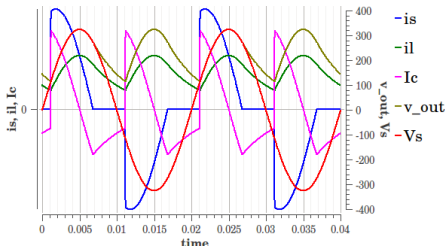
$$V_{s,peak} = 325, F=50 \text{ Hz}, r = 1k\Omega, c=5\mu.$$



- ▶ When diode is conducting, capacitor current leads supply voltage.
- ▶ When capacitor current is zero, $I_R = I_s$. Capacitor current slowly increases in negative direction.
- ▶ After sometime, $I_c = -I_R$, therefore supply current is zero and hence diode will stop conducting.
- ▶ Capacitor starts discharging, output voltage starts falling till diode start conducting again.

- ▶ Uncontrolled Rectifiers
 - ▶ Single phase diode rectifier with R, RL and RC loads.
 - ▶ Three phase diode rectifier with R, RL and RC loads.

Next Class

- ▶ AC/DC Converter - Phase Controlled Rectifiers
- ▶ Thank you!!

For Further Reading:

- ▶ Power Electronics: Converters, Applications, and Design: N. Mohan, T. M. Undeland, W. P. Robbins, John Wiley and Sons.
- ▶ Power electronics and motor drives: advances and trends: Bimal K Bose. Pearson Education.