



EN 206
1/19

Prof. Doolla

Introduction

Analysis

EN 206 - Power Electronics and Machines

Transformers

Suryanarayana Doolla
Department of Energy Science and Engineering
Indian Institute of Technology, Bombay
suryad@iitb.ac.in



Lecture Organization - Modules

EN 206
2/19

Prof. Doolla

Introduction

Analysis

- Introduction and Power Semiconductor Switches
- **Module 1: Transformers**
- Module 2: AC/DC converter / Rectifier
- Module 3: DC machines and Drives
- Module 4: DC/DC converter
- Module 5: Induction Machine
- Module 6: DC/AC converter / Inverter
- Module 7: AC/AC converter / Cyclo converter
- Module 8: Synchronous Machine
- Module 9: Special Topics: Machines, HVDC, APF



Definition

EN 206
3/19

Prof. Doolla

Introduction

Analysis

- Transformer is a device or a machine, that transfers electrical energy from one electrical circuit to another electrical circuit through the medium of magnetic field and without change in frequency.
- It is possible to step up or step down the voltage/current of a transformer, but the frequency remains constant.



Types of Transformers

EN 206
4/19

Prof. Doolla

Introduction

Analysis

Voltage Level

- Step Up
- Step Down
- Isolation

Construction

- Core
- Shell

Application

- Power Transformer
- Distribution Transformer
- Generation Transformer

Connection

- Star-Star, Star-Delta
- Delta-Delta, Delta-Star

The principle of operation remains the same, irrespective of voltage level, type, size and usage pattern.



Distribution Transformers

EN 206
5/19

Prof. Doolla

Introduction
Analysis

Pole Mounted



Features

- Ratings: CRGO Silicon Steel Transformers - Upto 167 kVA, Amorphous Metal Transformers - Upto 167 kVA
 - Cooling : ONAN, OA
-
- Primary voltage (Upto 33 kV), Secondary Voltage (120, 120/240, 210-105, 250, 240/480 V)
 - Winding material : Copper / Aluminium
 - Tapping range : 5% in steps of 2.5%



Power Transformers

EN 206
6/19

Prof. Doolla

Introduction

Analysis

Power Transformer



Features

- Small (10-25MVA, 12-66kV)
 - Medium (Up to 30 MVA, Up to 132 kV)
 - Large (25 to 500 MVA, 11 to 765 kV)
-
- Cooling: ONAN, ONAF
 - Winding material : Copper




Construction

EN 206
7/19

Prof. Doolla

Introduction

Analysis

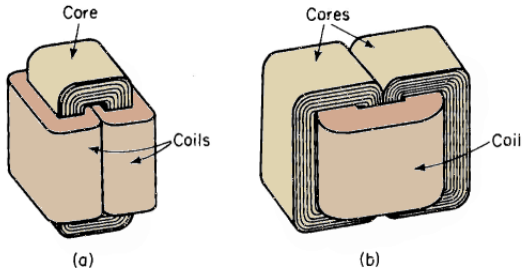

- Core type : Winding surrounds majority part of the core; concentric coil type
- Shell type: Core surrounds majority part of the winding, interleaved or sandwich type
- For a given output and voltage rating, core-type transformer requires less iron but more conductor material as compared to shell-type material



Construction

EN 206
8/19

Prof. Doolla

Introduction

Analysis

- Magnetic core: Stack of thin silicon-steel laminations, about 0.35mm thick for 50 Hz transformers
- Cold-rolled grain oriented sheet - Steel (CRGO): Low core loss and high permeability. Typically used in large power and distribution transformers
- Amorphous Steel: Core loss one third of conventional steel. Typically used in distribution transformers




Ideal Transformer

EN 206
9/19

Prof. Doolla

Introduction

Analysis

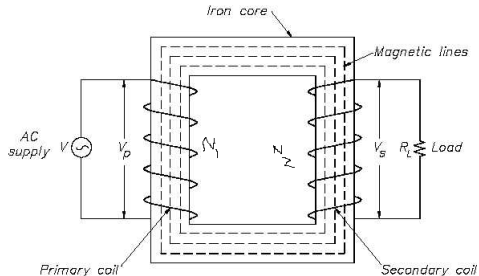

- Winding resistances are negligible.
- All flux setup by primary links the secondary.
- Core has constant permeability.
- The core losses (hysteresis and eddy current) are negligible.
- The magnetizing current and hence flux are sinusoidal in nature.



Ideal Transformer- EMF Generation

EN 206
10/19

Prof. Doolla

Introduction

Analysis

- EMF induced in the primary $e_1 = -N_1 \frac{d\phi}{dt}$
- If we assume that the flux is sinusoidal in nature ($\phi = \phi_m \sin \omega t$), then:
$$e_1 = -N_1 \omega \phi_m \cos \omega t = N_1 \omega \phi_m \sin(\omega t - \frac{\pi}{2})$$
- Rms value of $e_1 = E_1 = \frac{E_{1,max}}{\sqrt{2}} = \frac{N_1 \omega \phi_m}{\sqrt{2}} = \sqrt{2} \pi f N_1 \phi_m$
- EMF induced in the secondary
$$e_2 = -N_2 \frac{d\phi}{dt} = -N_2 \omega \phi_m \cos \omega t = E_{2,max} \sin(\omega t - \frac{\pi}{2})$$
- Rms value of $e_2 = E_2 = \frac{E_{2,max}}{\sqrt{2}} = \frac{N_2 \omega \phi_m}{\sqrt{2}} = \sqrt{2} \pi f N_2 \phi_m$

$\therefore \frac{E_1}{E_2} = \frac{N_1}{N_2}$, also $\frac{E_1}{N_1} = \frac{E_2}{N_2} = \sqrt{2} \pi f N_2 \phi_m$, i.e, emf per turn in primary is equal to emf per turn in secondary.




Ideal Transformer- No Load - Phasor Diagram

EN 206
11/19

Prof. Doolla

Introduction

Analysis

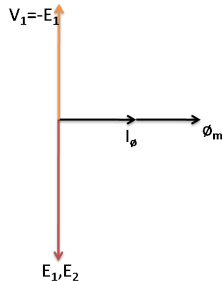

- The core flux (ϕ_m) lags the induced emf (E_1 , E_2) by 90°
- The no load current or magnetizing current (I_ϕ) is in phase with the core flux (ϕ_m)
- Supply voltage leads the magnetizing current (I_ϕ) and core flux (ϕ_m) by 90° , as the system is purely inductive.




Ideal Transformer- Phasor Diagram - Secondary loaded

EN 206
12/19

Prof. Doolla

Introduction

Analysis

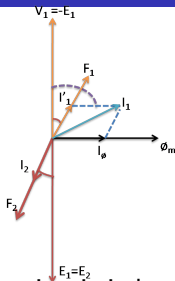

- When the secondary circuit is loaded, secondary mmf being opposite to ϕ_m , tends to reduce the alternating mutual flux ϕ_m .
- For an ideal transformer $|E_1| = |V_1|$, as the supply voltage remains constant, therefore more amount of power is drawn from primary.
- Compensating primary mmf = Secondary mmf i.e., $I'_1 N_1 = I_2 N_2$, where I'_1 is load component of primary current I_1 .



Ideal Transformer- Phasor Diagram - Secondary loaded

EN 206
13/19

Prof. Doolla

Introduction

Analysis

- The total primary current I_1 is the phasor sum of I_1' and I_ϕ .
- $\overline{I_1} = \overline{I_1'} + \overline{I_\phi}$
- Power factor of the system is given by $\cos\phi$
- If I_ϕ is neglected, $I_1 N_1 = I_2 N_2 \implies \frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1} = \frac{V_1}{V_2}$
- Total input power = Total output power $\implies V_1 I_1 = V_2 I_2$



Impedance Transformation

EN 206
14/19

Prof. Doolla

Introduction

Analysis

- Used to simplify the equivalent circuit
- If Z_2 is impedance of load connected, V_2 is the voltage of secondary, I_2 is current through the secondary winding, then $Z_2 = \frac{V_2}{I_2}$,
- Also, $\frac{V_1}{N_1} = \frac{V_2}{N_2}$; $I_1 N_1 = I_2 N_2$
- If the secondary impedance is transferred to primary side, then impedance seen by primary circuit is given by:
- $\frac{V_1}{I_1} = \frac{N_1}{N_2} V_2 \times \frac{N_1}{N_2} \frac{1}{I_2} \implies \frac{V_1}{I_1} = Z_2' = \left(\frac{N_1}{N_2}\right)^2 Z_2$
- Similarly, when primary impedance is referred to secondary, $Z_1' = \left(\frac{N_2}{N_1}\right)^2 Z_1$




Phasor Diagram - No Load

EN 206
15/19

Prof. Doolla

Introduction


Analysis

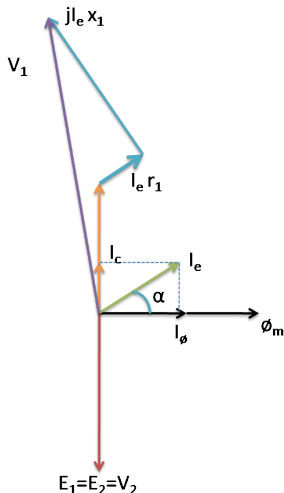

- α : Hysteresis angle, I_e : exciting current, I_ϕ : Magnetizing current, I_c : Core loss component
- r_1 : primary resistance
- x_1 : fictitious quantity introduced to represent the leakage flux in primary
- Primary leakage impedance drop is about 2 to 5% even at full load.
- The magnetizing current is typically 1% of full load current and hence is neglected.



EN 206
16/19

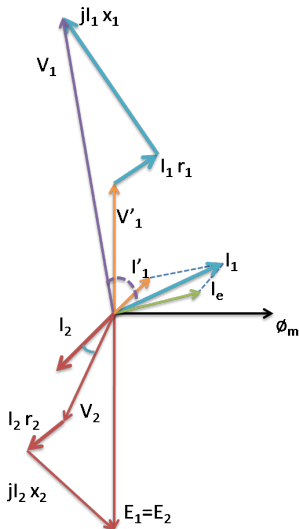



Equivalent Circuit


EN 206
17/19

Prof. Doolla


Introduction

Analysis

With Exciting current neglected:

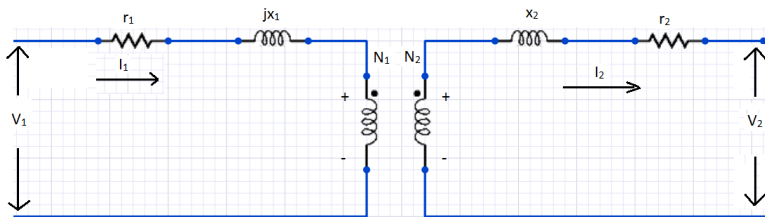

Exact equivalent circuit:

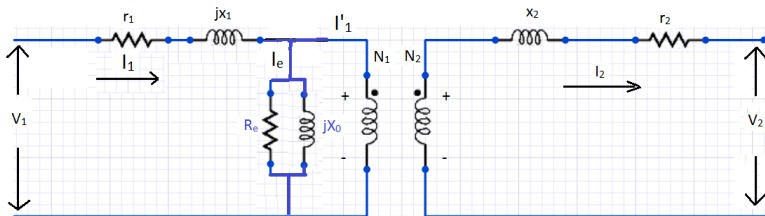



Equivalent Circuit


EN 206
18/19

Prof. Doolla

Introduction

Analysis

Equivalent circuit referred to primary:

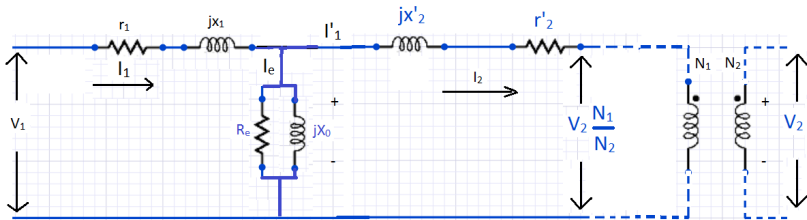



Summary

EN 206
19/19

Prof. Doolla

Introduction

Analysis

- Transformers
 - Principle of operation
 - Equivalent Circuit

Next Class

- Testing of Transformer
 - Auto Transformer
- Thank you!!

For Further Reading:

- Transformer Engineering: Design and Practice Authors: S.V. Kulkarni and S.A. Khaparde Publisher: Marcel Dekker (Taylor & Francis Group), New York, May 2004 ISBN: 0-8247-5653-3
- Electric Machinery: A. E. Fitzgerald, C. Kingsley, S. D. Umans. Publisher: TMH, New Delhi, India, 2009